

Midterm

Apr. 26, 2021

Time: 10:30 ~ 11:50

Name _____


Student ID _____

Signature _____

- If there is no answer, you can get only partial credit for your work.
- Don't forget the units of your answers

1. (15 points)

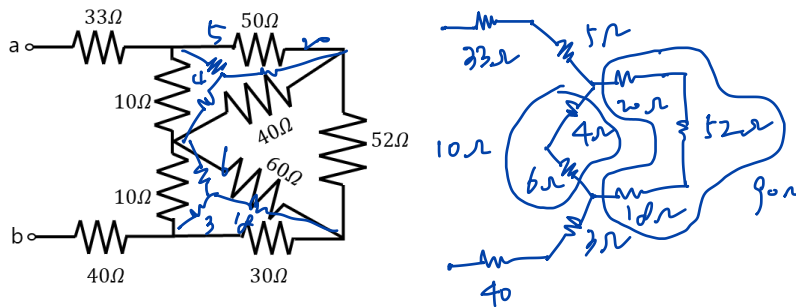(a) (5 points) Find the resistance between terminals a-b in the following circuit.




$$\frac{1}{R_p} = \frac{1}{10} + \frac{1}{60} = \frac{9+1}{90} = \frac{1}{9}$$

$$R_{eq} = 33 + 5 + 9 + 3 + 40.$$

Ans: 90Ω

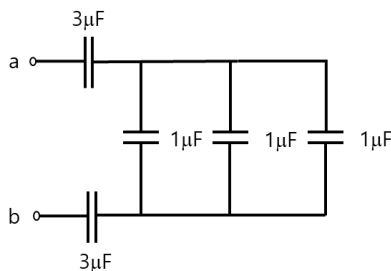
(b) (5 points) Find the capacitance between terminals a-b in the following circuit.




$$\frac{1}{C} = \frac{1}{3\mu} + \frac{1}{3\mu} + \frac{1}{3\mu} = \frac{1}{1\mu}$$

Ans: 1μF

(c) (5 points) Find the inductance between terminals a-b in the following circuit.

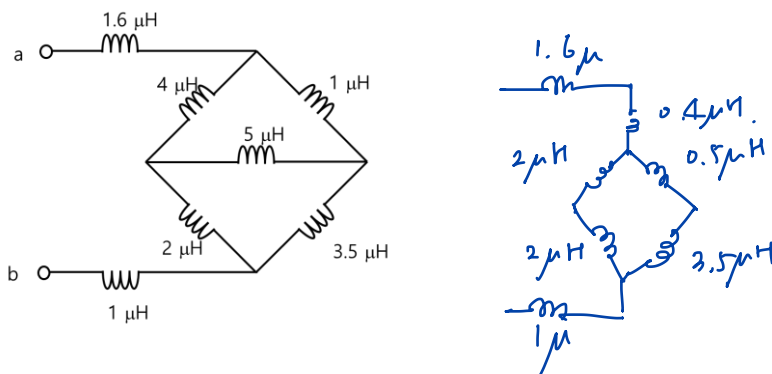Ans: 5μH

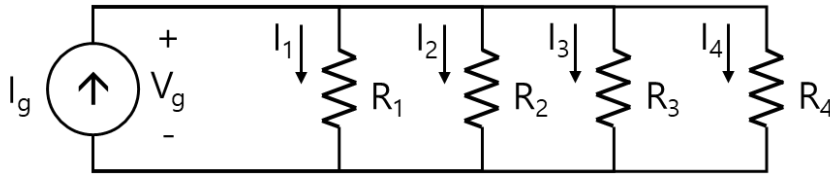2. (10 points) When $I_g = 8\text{mA}$, $V_g = 1\text{V}$, $I_1 = 2I_2$, $I_2 = 10I_3$, and $I_3 = I_4$, find R_1 , R_2 , R_3 , and R_4 in the following circuits.



$$32I_4 = 8\text{mA} \quad \therefore I_4 = 0.25\text{mA}$$

$$\therefore R_4 = \frac{1}{0.25\text{mA}} = \frac{1000}{0.25} = 4\text{k}\Omega$$

$$R_3 = 4\text{k}\Omega$$

$$R_2 = \frac{1}{2.5\text{mA}} = \frac{1000}{2.5} = 400\Omega$$

$$R_1 = \frac{1}{5\text{mA}} = \frac{1000}{5} = 200\Omega$$

$$\frac{1}{4\text{k}} = 0.25\text{mA}$$


$$\frac{1}{4\text{k}} = 0.25\text{mA}$$

$$\frac{1}{400} = 2.5\text{mA}$$

$$\frac{1}{200} = 5\text{mA}$$

Ans: $R_1 = 200\Omega$, $R_2 = 400\Omega$, $R_3 = 4\text{k}\Omega$, $R_4 = 4\text{k}\Omega$

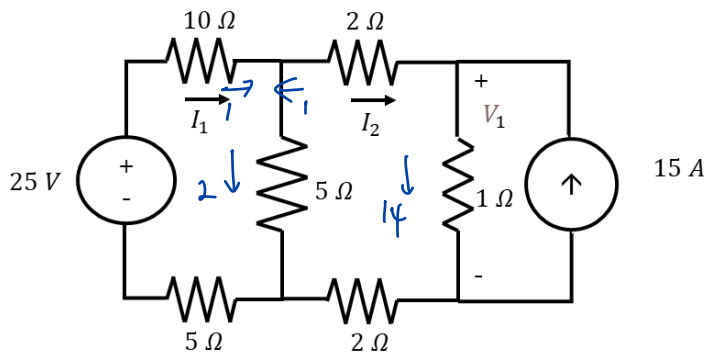3. (10 points) Find V_1 , I_1 , and I_2 .



$$10I_1 + 5(I_1 - I_2) + 5I_1 = 25$$

$$2I_2 + (I_2 + 15) + 2I_2 + 5(I_2 - I_1) = 0$$

$$20I_1 - 5I_2 = 25$$

$$-5I_1 + 10I_2 = -15$$

$$+ | 40I_1 - 10I_2 = 50$$


$$35I_1 = 35$$

$$\therefore I_1 = 1\text{A}$$

$$I_2 = -1\text{A}$$

Ans: $V_1 = 14\text{V}$, $I_1 = 1\text{A}$, $I_2 = -1\text{A}$

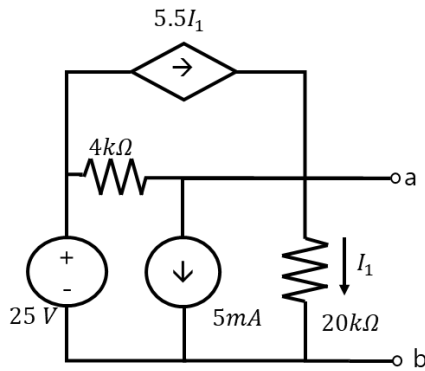4. (15 points) Find the Thevenin equivalent circuit between terminal a-b of the following circuit.




For V_{oc} .
$$\frac{V_{oc}-25}{4k} + 5m + \frac{V_{oc}}{20k} - 5.5 \frac{V_{oc}}{20k} = 0.$$

$$5V_{oc} - 125 + 100 + V_{oc} - 5.5V_{oc} = 0$$

$$0.5V_{oc} = 25$$

$$\therefore V_{oc} = 50V.$$


For I_{sc}

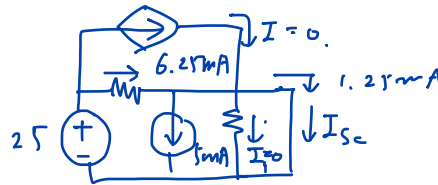


$$I_{sc} = 1.25mA.$$

$$I_{sc} = \frac{25}{4k} - 5m = 6.25m - 5m = 1.25mA$$
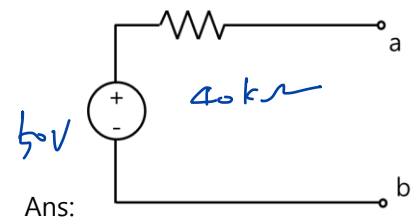
$$R_{Th} = \frac{50}{1.25m} = 40k\Omega$$



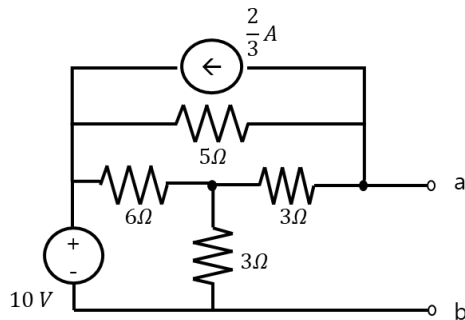5. (10 points) Find the Norton equivalent circuit between terminal a-b of the following circuit.



For V_{oc}
$$\frac{V_1 - 10}{6} + \frac{V_1}{3} + \frac{V_1 - V_{oc}}{3} = 0.$$

$$\frac{V_{oc} - V_1}{3} + \frac{V_{oc} - 10}{5} + \frac{2}{3} = 0.$$

$$V_1 - 10 + 2V_1 + 2V_1 - 2V_{oc} = 0 \Rightarrow 5V_1 - 2V_{oc} = 10.$$



$$5V_{oc} - 5V_1 + 3V_{oc} - 3 \cdot 0 + 10 = 0 \Rightarrow -5V_1 + 8V_{oc} = 20$$

$$\therefore V_{oc} = 5V.$$


For I_{sc}

$$\frac{V_2 - 10}{6} + \frac{V_2}{3} + \frac{V_2}{3} = 0$$
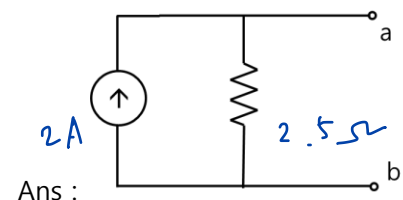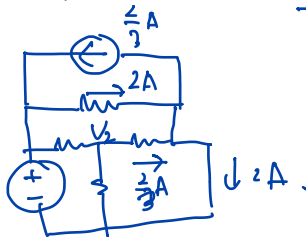
$$V_2 - 10 + 2V_2 + 2V_2 = 0 \Rightarrow V_2 = 2V.$$



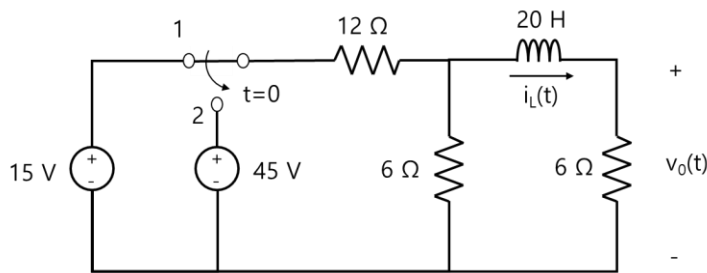6. (10 points) In the following circuit, the switch is moved from terminal 1 to 2 at $t=0$.




- (a) (3 points) Find $i_L(t < 0)$.

$$R = 12 + 3 = 15\Omega$$

$$\bar{i} = 1A. \quad \bar{i}_L(t < 0) = \frac{1}{2} \cdot \bar{i} = 0.5A$$

- (b) (7 points) Find $v_o(t > 0)$.

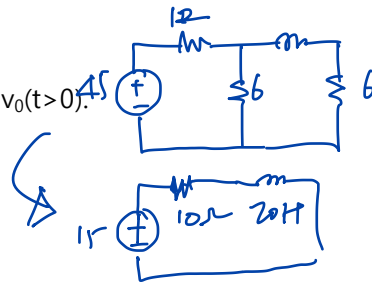


$$\text{Ans: } i_L(t < 0) = 0.5A$$

$$i_L(t > 0) = K_1 + K_2 e^{-t/2}$$

$$= 1.5 - e^{-t/2}$$

$$\text{Ans: } v_o(t > 0) = (9 - 6e^{-t/2})V$$

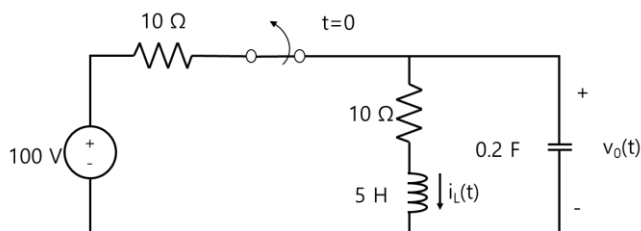7. (15 points) In the following circuit, the switch is open at $t=0$.



- (a) (3 points) Find $i_L(t < 0)$ and $v_o(t < 0)$.

$$\text{Ans: } i_L(t < 0) = 5A, \quad v_o(t < 0) = 50V$$

- (b) (8 points) Find $i_L(t > 0)$.

$$5 \frac{d\bar{i}_L}{dt} + 10 \cdot \bar{i}_L + \frac{1}{0.2} \int_{-\infty}^t \bar{i}_L(\tau) d\tau = 0$$

$$\frac{d^2 \bar{i}_L}{dt^2} + 2 \bar{i}_L + \bar{i}_L = 0$$

$$s^2 + 2s + 1 = 0 \quad \therefore s = -1$$

$$i_L(t) = K_1 e^{-t} + K_2 t e^{-t} \quad i_L(t=0) = 5A \quad \therefore K_1 = 5$$

$$v_o(t) = 10 \cdot i_L + 5 \cdot \frac{d\bar{i}_L}{dt} = 10(K_1 e^{-t} + K_2 t e^{-t}) + 5(-K_1 e^{-t} + K_2 e^{-t} - K_2 t e^{-t})$$

$$v_o(t=0) = 10K_1 + 5(-K_1 + K_2) = 50$$

$$\therefore K_1 = K_2$$

$$(5e^{-t} + 5te^{-t})A$$

$$\text{Ans: } i_L(t > 0) =$$


(c) (4 points) Find $v_o(t>0)$.

$$v_o(t) = 50e^{-t} + 50te^{-t} + 5 \left(-\cancel{e^{-t}} + 5\cancel{e^{-t}} - 5te^{-t} \right) \\ = 50e^{-t} + 25te^{-t}$$

Ans: $v_o(t>0) = \underline{(50e^{-t} + 25te^{-t}) \text{ V}}$


8. (15 points)

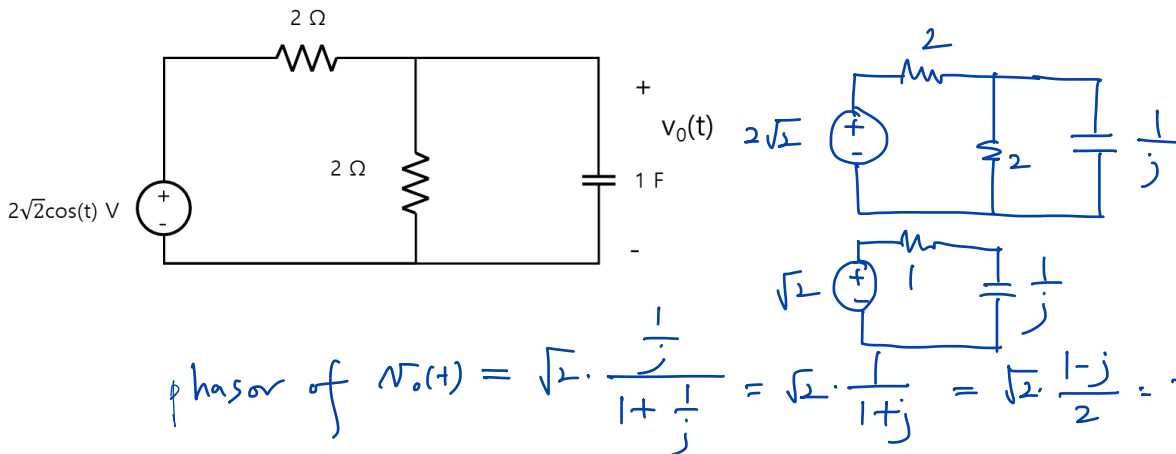(a) (10 points) In the following circuit, we want to find the voltage in steady state using phasor. Find the phasor of $v_o(t)$ and $v_o(t)$. ($\frac{1+j}{\sqrt{2}} = e^{j45^\circ}$, $\frac{1-j}{\sqrt{2}} = e^{-j45^\circ}$)



Ans: phasor of $v_o(t) = \underline{e^{-j45^\circ} \text{ V}}$, $v_o(t) = \underline{\cos(t - 45^\circ) \text{ V}}$

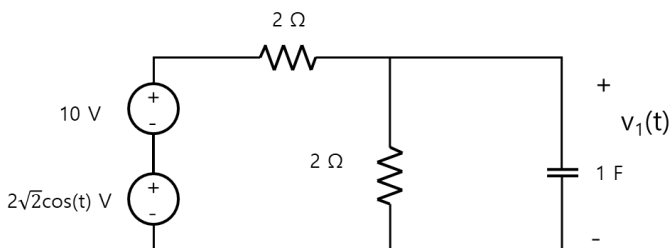(b) (5 points) In the following circuit, we want to find the voltage, $v_1(t)$ in steady state using superposition principle.



Ans: $v_1(t) = \underline{5 + \cos(t - 45^\circ) \text{ V}}$