
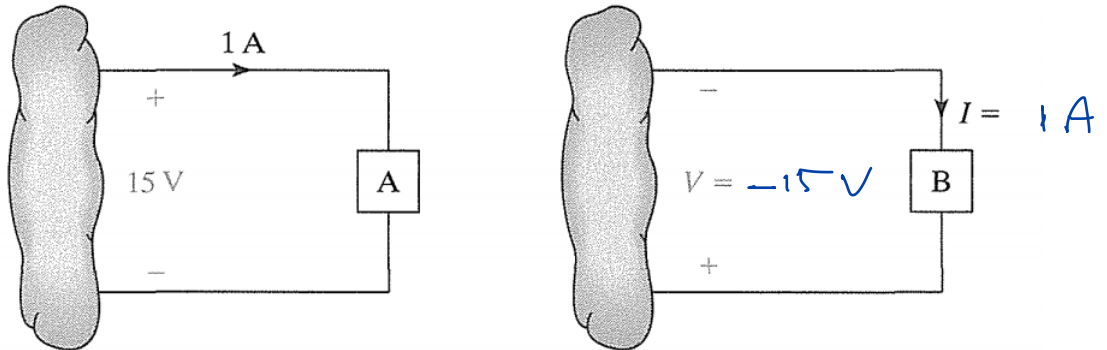


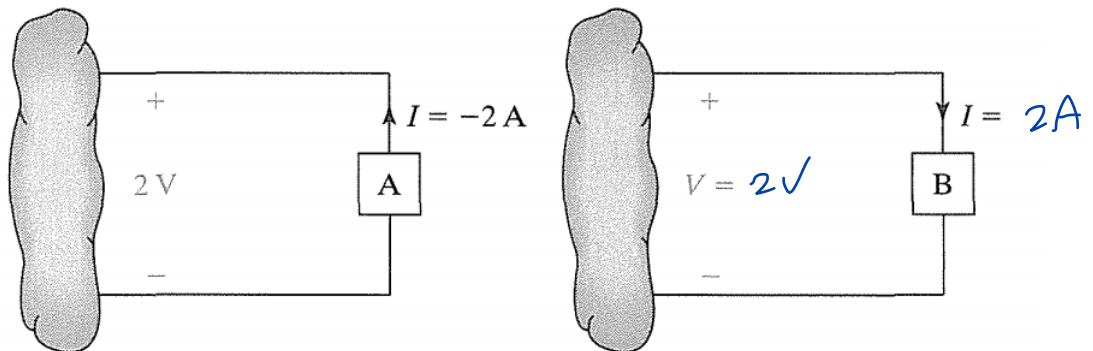
1. Assign values to  $V$  and  $I$  in element B so that it is equivalent to element A (see Figure 1).



(a)




(b)

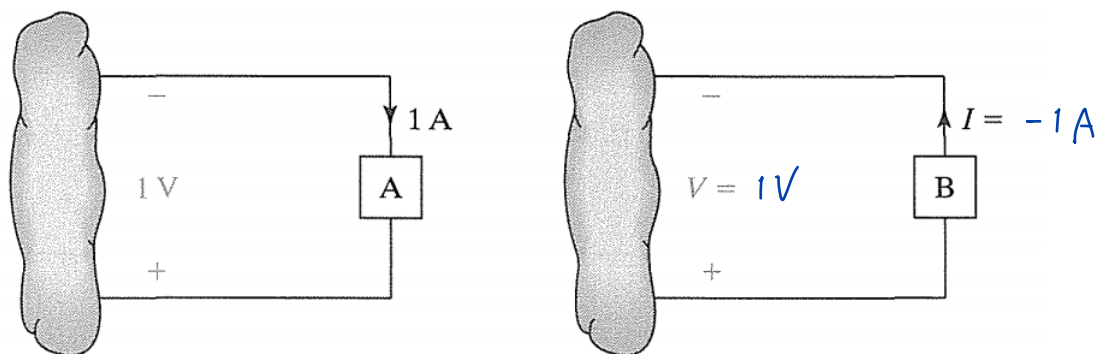


(c)

Figure 1

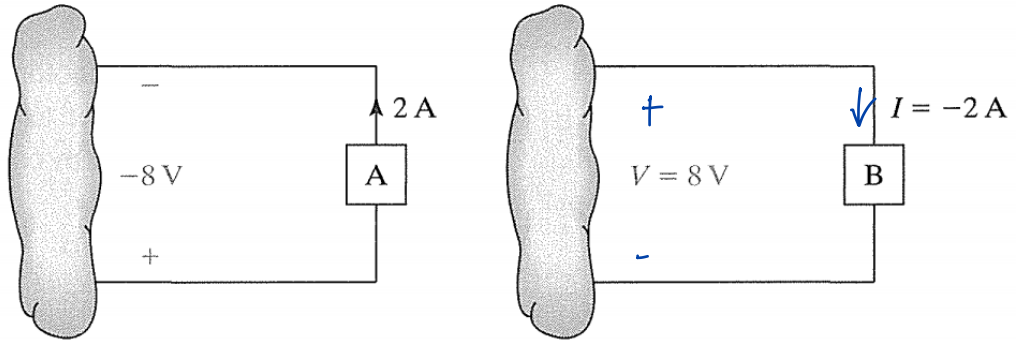
2. Assign directions to currents and polarities to voltages in element B so it is equivalent to element A (see Figure 2)



(a)

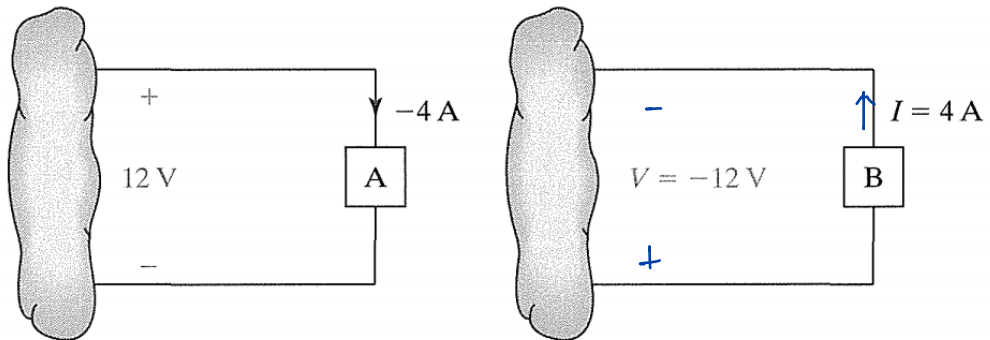

(b)

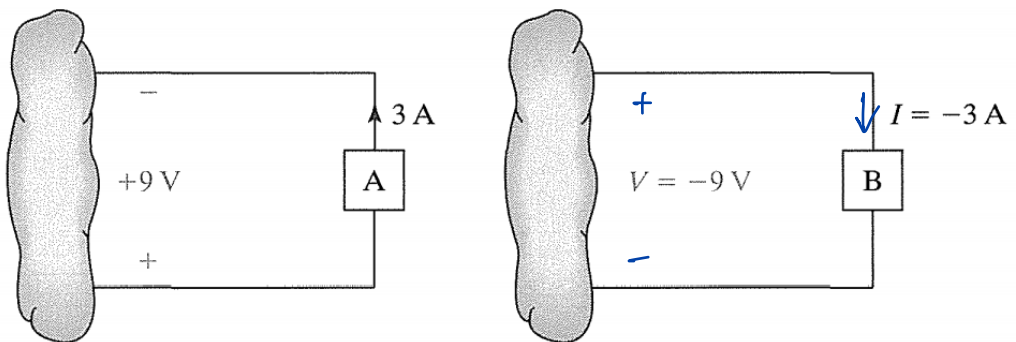

(c)

Figure 2

3. In the elements of Figure 3, determine for each if they are supplying power or absorbing power and the magnitude of the power being transferred.

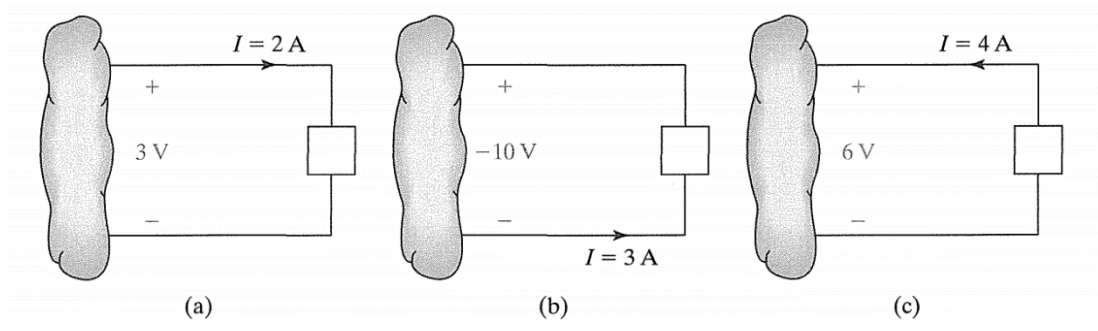


Figure 3

absorbing

absorbing

supplying .

4. In Figure 4 determine for each element whether it is supplying or absorbing power. If all the energy absorbed is dissipated as heat dissipated (in joules) over a period of one hour for each of the circuits shown.

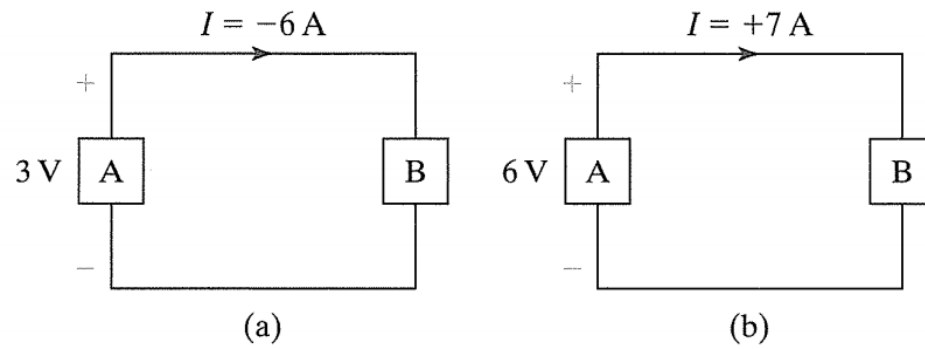


Figure 4

A: absorbing  
B: supplying

A: supplying  
B: absorbing

5. A heater element draws 2.0 A when connected to a 120 V source. Calculate both the resistance of the element and the power absorbed in the form of heat.

$$I = 2 \text{ A}.$$

$$V = 120 \text{ V}.$$

$$\text{Resistance} = 60 \Omega$$

$$\text{Power} = 240 \text{ W}.$$

6. A speaker is a device that converts electrical energy into sound energy. Assume the internal resistance of a speaker is typically  $8\Omega$ . The speaker's power rating is maximum power that can be delivered to it without damage. Therefore, determine the maximum safe current that can be delivered to a stereo speaker with internal resistance of  $8\Omega$  and a power rating of 200 watts.

$$I^2 R \leq 200 \text{ W.}$$

$$I^2 \leq 25$$

$$\therefore \underline{5 \text{ A}}$$

7. Find  $I$  and  $V_0$  in the network in Figure 5.

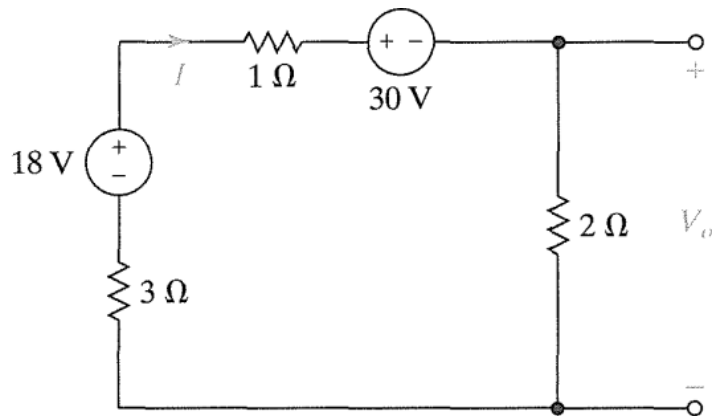


Figure 5

$$-18 + I + 30 + 2I + 3I = 0$$

$$6I = -12$$

$$\therefore I = -2A.$$

$$\therefore V_0 = 2 \cdot I = -4V.$$

8. Find  $V$ ,  $I_1$ ,  $I_2$ , and  $P_{6\Omega}$  in the network in Figure 6.

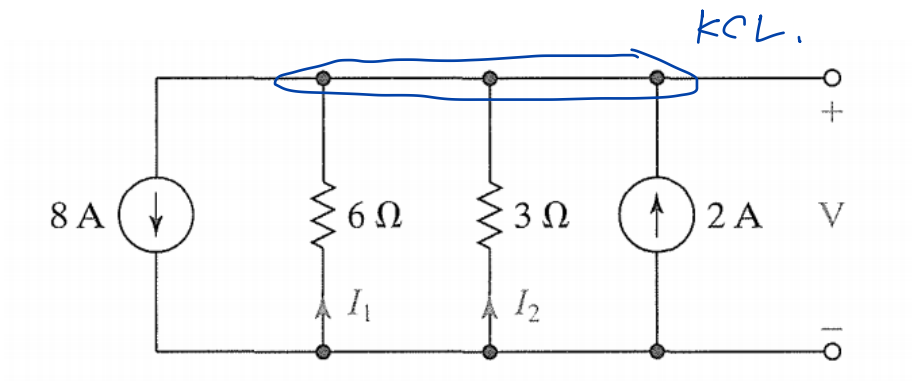


Figure 6

$$\frac{V}{6} + \frac{V}{3} + 0 - 2 = 0$$

$$\frac{V}{6} + \frac{V}{3} = -6$$

$$V + 2V = -36$$

$$\therefore V = -12V$$

$$I_1 = \frac{-V}{6} = 2A$$

$$I_2 = \frac{-V}{3} = 4A$$

$$P_{6\Omega} = I_1^2 R = 24W$$



9. Find the equivalent resistance at the terminals  $A - B$  in the network in Figure 7.


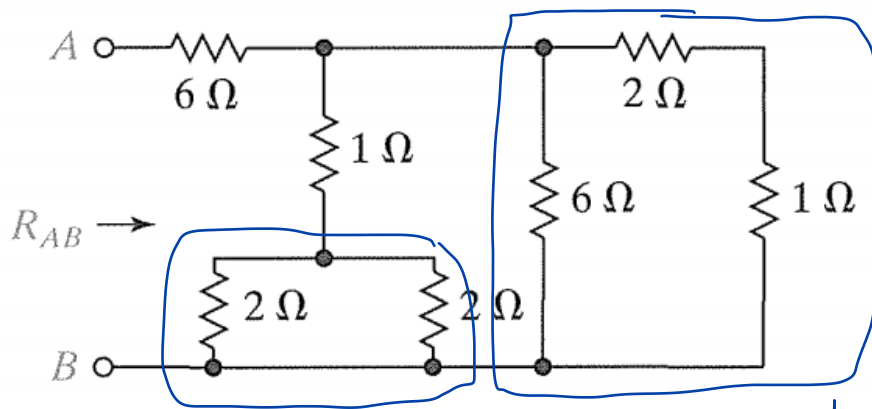


Figure 7


$$\frac{1}{R_p} = \frac{1}{6} + \frac{1}{3} = \frac{1+2}{6}$$

$$\therefore R_p = 2\Omega$$

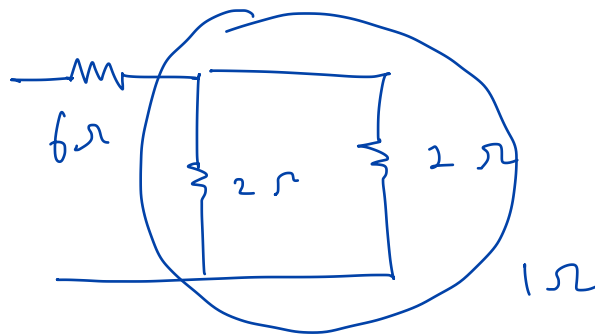



$$\therefore R_{AB} = 7\Omega$$

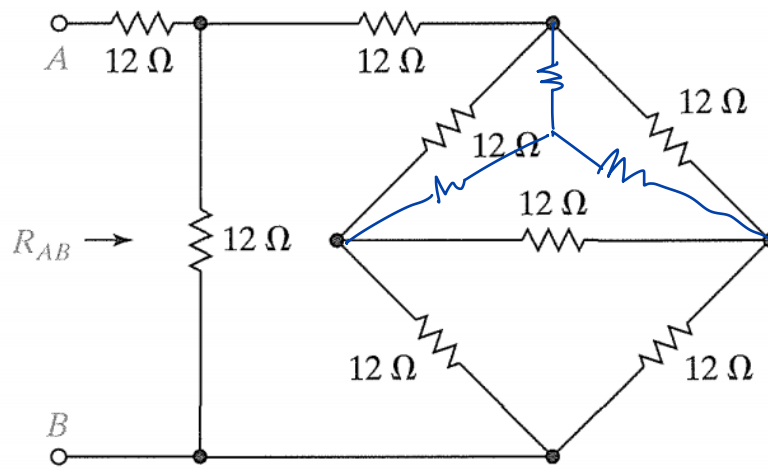10. Find the resistance at terminals  $A - B$  in the network in Figure 8



$$\frac{12 \cdot 12}{36} = 4\Omega$$

Figure 8

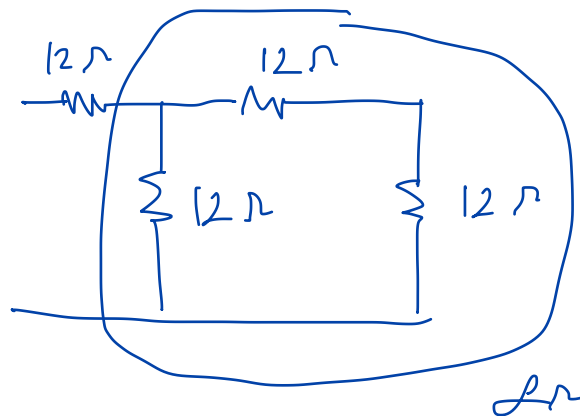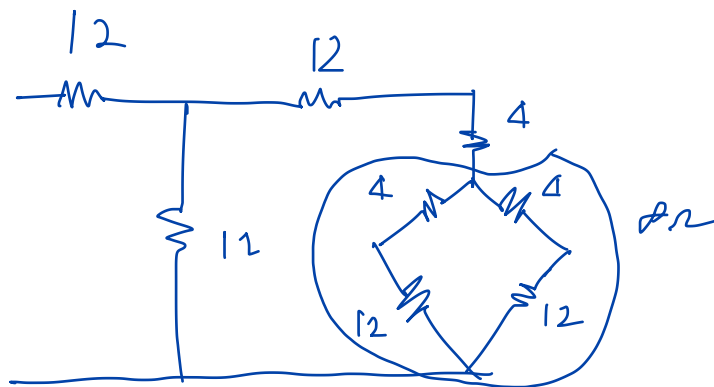

$$\begin{aligned} \frac{1}{R_p} &= \frac{1}{12} + \frac{1}{24} \\ &= \frac{2+1}{24} = \frac{1}{8} \end{aligned}$$

$$\therefore R_{AB} = 20\Omega$$