

Midterm


Apr. 23, 2019
Time: 10:30 ~ 11:50

Name _____
ID Number _____
Signature _____

- If there is no answer, you can get only partial credit for your work.
- Don't forget the units of your answers

1. (20 points) Find voltages, currents and powers in the following circuits.

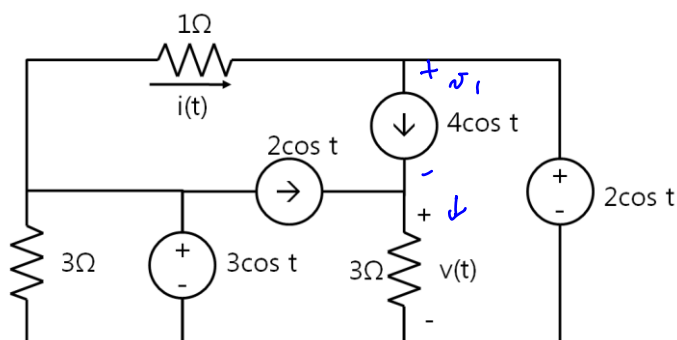
(a) (10 points) Find $v(t)$, $i(t)$ and $p(t)$ at a current source of $4\cos(t)$ in the following circuits.



$$v_1 = -16\cos t$$

Ans: $v(t) = 18\cos t (V)$, $i(t) = \cos t (A)$, $p(t)$ at a current source of $4\cos(t) = -64\cos^2 t (W)$

(b) (5 points) Find v .

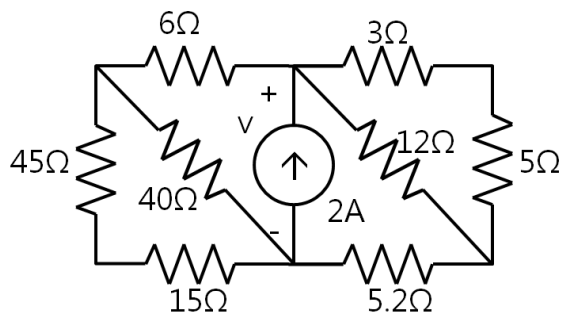

Ans: $v = 15V$

(c) (5 points) Find v .

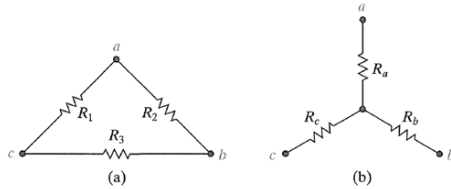
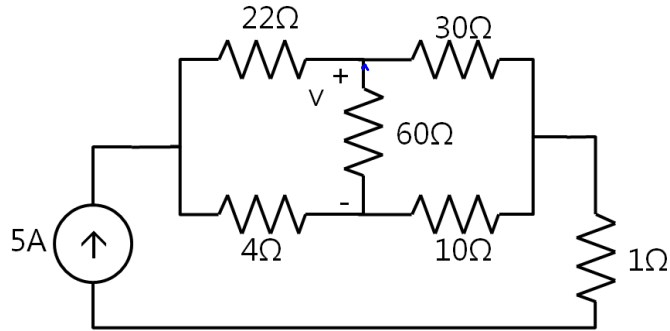


FIGURE 2.20 Δ and Y resistance networks.

$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

$$R_1 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_b}$$


$$R_2 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_c}$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_a}$$

Ans: $v = -6V$


2. (20 points)

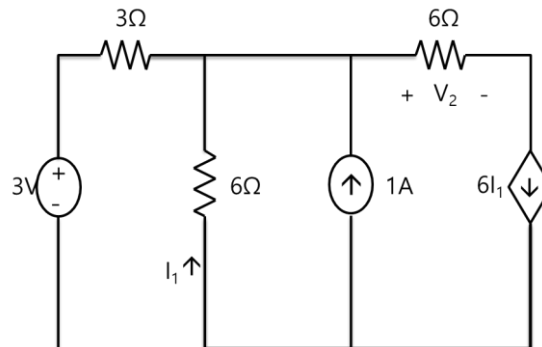(a) (10 points) In the following circuit, find i_1 and the power absorbed or supplied by the voltage source of 3V. (If $P < 0$, the power is supplied. If $P > 0$, the power is absorbed.)



Ans: $i_1 = \frac{2}{3} A$, $P_{3V} = -7W$


(b) (10 points) Find i_o .

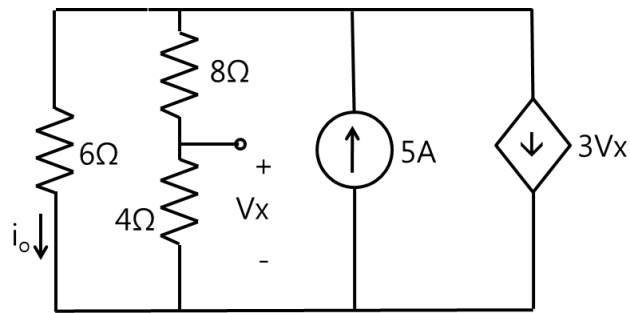

Ans: $i_o = \frac{2}{3} A$


3. (10 points)

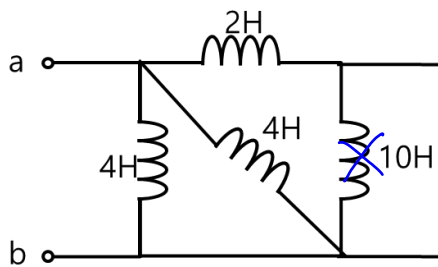(a) (5 points) Find the inductance between terminals a-b in the following circuit.





Ans.: $1 H$

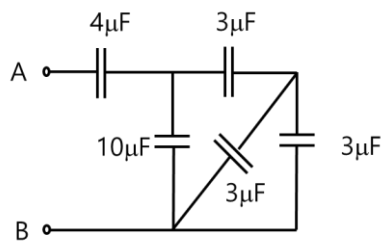(b) (5 points) Find the capacitance between terminals A-B in the following circuit.





Ans.: $3\mu F$

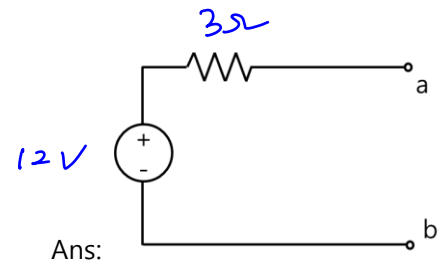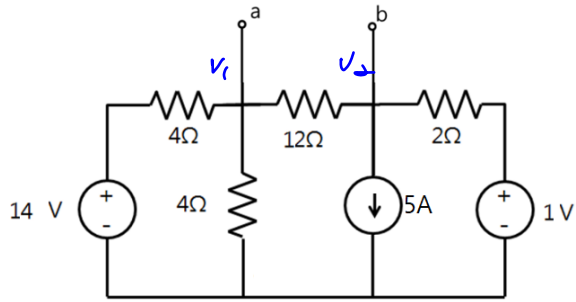
4. (10 points) Find the Thevenin equivalent circuit between terminal a-b of the following circuit.



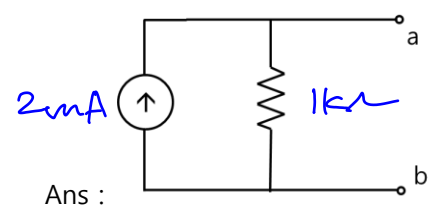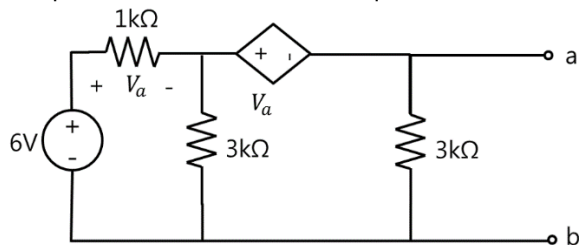
5. (10 points) Find the Norton equivalent circuit between terminal a-b of the following circuit.



6. (20 points)

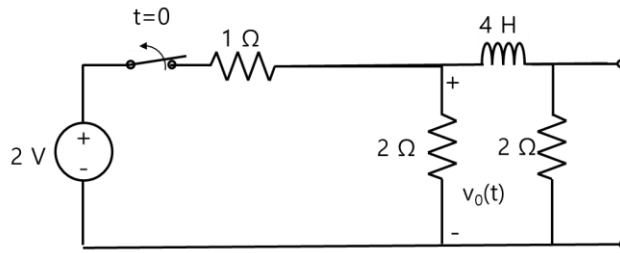
(a) (10 points) Find $v_0(t)$ for $t > 0$.

Ans: $v_0(t) = -e^{-t} (V)$

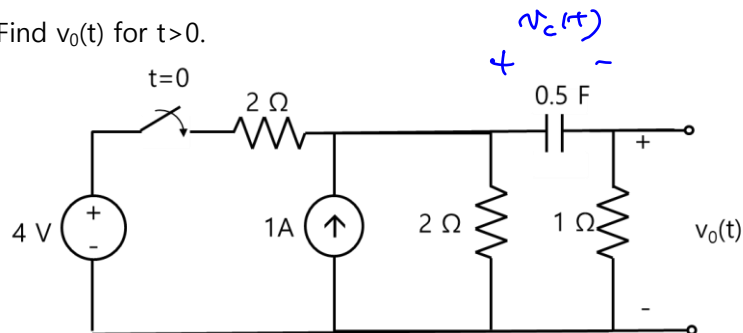(b) (10 points) Find $v_0(t)$ for $t > 0$.

Ans: $v_0(t) = 0.5e^{-t} (V)$

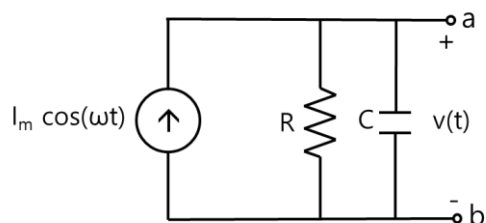7. (10 points) In the following circuit, a sinusoidal current source is applied. We want to find the steady-state $v(t)$.



- (a) (3 points) Using Kirchhoff's current law, Find the 1st order differential equation about $v(t)$.

$$\frac{v(t)}{R} + C \cdot \frac{dv}{dt} = I_m \cos \omega t$$

Ans: _____

- (b) (7 points) Assume that $v(t) = V_m \cos(\omega t + \theta)$. Express V_m and θ in terms of I_m , R , and C .

$$(a \cos x + b \sin x = R \cos(x - \alpha) \text{ where } R = \sqrt{a^2 + b^2}, \quad \tan \alpha = \frac{b}{a})$$

$$\text{Ans: } V_m = \frac{I_m}{\sqrt{\frac{1}{R^2} + \omega^2 C^2}}, \quad \theta = -\tan^{-1}(\omega RC)$$