

Example

D7.1. Determine the transfer function $\frac{V_0}{V_1}(j\omega)$ for the circuit in Figure D7.1 and locate the poles and zeros of the function.

$$\frac{V_o}{V_i}(j\omega) = \frac{4}{(j\omega)^2 + 5j\omega + 4}$$

① no zeros

② poles: $j\omega = -1, -4$

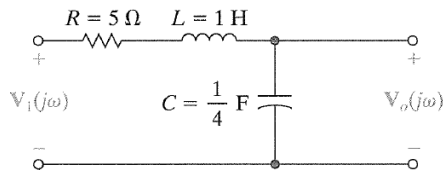



FIGURE D7.1

Ans: $\frac{V_0}{V_1}(j\omega) = \frac{4}{(j\omega)^2 + 5j\omega + 4}$, there are no zeros and the pole locations are $j\omega = -1$ and $j\omega = -4$.

Example

D7.2. Design a simple RC high-pass filter with a break frequency of 20 kHz. Use a resistor value of 1 k Ω .

Ans: $C = 8 \text{ nF}$.

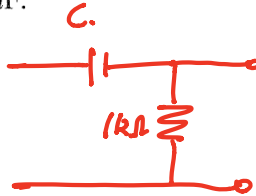

$\frac{1}{RC}$

$$\omega_{3dB} = 2\pi \cdot 20 \text{ kHz}$$

$$C = \frac{1}{2\pi \cdot 20 \text{ kHz} \cdot 1 \text{ k}\Omega}$$

$$= \frac{1}{40\pi \cdot 10^6} = 8 \text{ nF}$$

Example

D7.3. Determine the half-power frequency for each of the filters in Figure D7.3 and identify the type of filter.

(a) Low Pass Filter.

$$\omega_{H2} = \frac{1}{T} = \frac{1}{R_1 C} = \frac{1}{10 \times 20 \times 10^{-6}}$$

$$= 5 \times 10^3 \text{ rad/s}$$

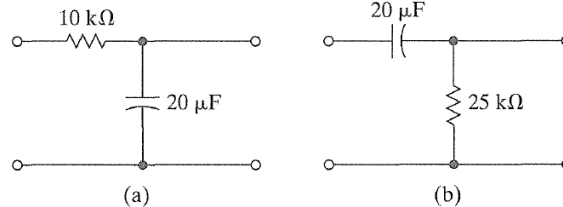


FIGURE D7.3

(b) High Pass Filter

$$\omega_{LO} = \frac{1}{T} = \frac{1}{R_1 C} = \frac{1}{25 \times 10^3 \times 20 \times 10^{-6}}$$

$$= 2 \text{ rad/s}$$

Ans: (a) Low-pass filter, $\omega_{HI} = 5 \text{ rad/s}$; (b) high-pass filter $\omega_{LO} = 2 \text{ rad/s}$.

Example

D7.4. Given the network in Figure D7.4, find the value of C that will place the circuit in resonance at 1800 rad/s.

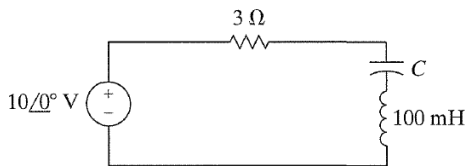


FIGURE D7.4

$$\omega = \frac{1}{\sqrt{LC}} = 1800 \text{ rad/s}$$

$$\omega C = \left(\frac{1}{1800}\right)^2, \quad C = \frac{1}{1800^2 \cdot L} = 3.09 \times 10^{-6} \text{ F}$$

Ans: $C = 3.09 \mu\text{F}$.

D7.5. Given the network in D7.4, determine the Q of the network and the magnitude of the voltage across the capacitor.

Ans: $Q = 60, |V_c| = 600 \text{ V}$.

$$V_c = 10 \times \frac{j\omega L}{3 + j\omega L + \frac{1}{j\omega C}}$$

$$= 600j = 600 \angle 90^\circ = \boxed{600 \text{ V}}$$

$$Q = 1800 \times \frac{L}{R} = 1800 \times \frac{100}{3} \times \frac{1}{1000}$$

$$= \boxed{60}$$

Example

$$BW = \frac{R}{L} = \frac{2\Omega}{40\text{mH}} = \frac{1000}{20} = 50 \text{ rad/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{40 \times 10^{-3} \times 100 \times 10^{-6}}} = 500 \text{ rad/s}$$

D7.6. A series RLC circuit is composed of $R = 2\ \Omega$, $L = 40\text{ mH}$, and $C = 100\ \mu\text{F}$. Determine the bandwidth of this circuit about its resonant frequency.

Ans: $BW = 50\text{ rad/s}$, $\omega_0 = 500\text{ rad/s}$.

D7.7. A series RLC circuit has the following properties: $R = 4\ \Omega$, $\omega_0 = 4000\text{ rad/s}$, and $BW = 100\text{ rad/s}$. Determine the values of L and C .

Ans: $L = 40\text{ mH}$, $C = 1.56\ \mu\text{F}$.

$$BW = \frac{R}{L} = 100 \quad L = \frac{4}{100} = 0.04\text{H} = 40\text{ mH.}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 4000 \quad \frac{1}{LC} = 4^2 \times 10^6$$

$$C = \frac{1}{4^2 \times 10^6 \times 40} = 1.56\ \mu\text{F}$$

Example

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 150}} = \frac{1}{\sqrt{3000}} = 577 \text{ rad/s}$$

$$BW = \frac{1}{RC} = \frac{1}{2 \times 10^3 \times 150 \times 10^{-6}} \approx 3.3 \text{ rad/s}$$

$$Q = \frac{\omega_0}{BW} = \frac{577}{3.3} \approx 173$$

D7.8. A parallel RLC circuit has the following parameters: $R = 2 \text{ k}\Omega$, $L = 20 \text{ mH}$, and $C = 150 \text{ }\mu\text{F}$. Determine the resonant frequency, the Q , and the bandwidth of the circuit.

Ans: $\omega_0 = 577 \text{ rad/s}$, $BW = 3.33 \text{ rad/s}$, $Q = 173$.

D7.9. A parallel RLC circuit has the following parameters:

$R = 6 \text{ k}\Omega$, $BW = 1000 \text{ rad/s}$, and $Q = 120$. Determine the values of L , C , and ω_0 .

Ans: $C = 0.167 \text{ }\mu\text{F}$, $L = 416.7 \text{ }\mu\text{H}$, $\omega_0 = 119760 \text{ rad/s}$.

$$\frac{\omega_0}{BW} = 120 \quad \omega_0 = 120 \times 1000 = 120000$$


$$C = \frac{1}{6000 \times 120000} = 0.167 \times \frac{1}{10^6} = 0.167 \text{ }\mu\text{F}$$

$$L = \frac{1}{C \cdot \omega_0^2} = \frac{6 \cdot 10^8}{12^2 \cdot 10^9} \approx 416.7 \text{ }\mu\text{H}$$

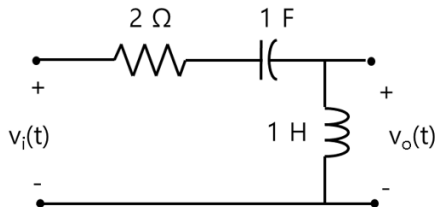Example

- Ex1

(10 points) In the following circuit, the input signal is $v_i(t)$ and the output signal is $v_o(t)$.



$$FR = \frac{j\omega}{2 + j\omega + \frac{1}{j\omega}} = \frac{(j\omega)^2}{(j\omega)^2 + 2j\omega + 1}$$

- (4 points) Find the frequency response of $V_o(j\omega)/V_i(j\omega)$.
- (4 points) Find the magnitude and phase of the frequency response from (a).
- (2 points) Find the magnitude of the frequency response at $\omega = 0$ rad/s, $\omega = 1$ rad/s, and $\omega = \infty$ rad/s.


(b) magnitude $\frac{\omega^2}{\sqrt{(\omega^2 - 1)^2 + 4\omega^2}}$, phase $= -\tan^{-1}\left(\frac{2\omega}{\omega^2 - 1}\right)$

(c) $\omega = 0$, $|FR| = 0$, phase $= 0$ $\omega = 1$, $|FR| = \frac{1}{2}$, phase $= 90^\circ$
 $\omega = \infty$, $|FR| = 1$, phase $= 0$

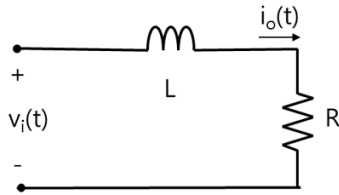Example

- Ex2

(10 points) Consider the following circuit. The input signal is $v_i(t)$ and the output signal is $i_o(t)$.



$$FR = \frac{1}{R + j\omega L}$$

- (a) (4 points) Find the frequency response, $I_o(j\omega)/V_i(j\omega)$.
- (b) (4 points) 3-dB bandwidth in the unit of Hz.
- (c) (2 points) Determine the type of the filter. (low-pass filter, high-pass filter, bandpass filter, or band-rejection filter)

$$(b) \quad \frac{1}{\sqrt{2}} \times \frac{1}{\sqrt{2}} = \text{Magnitude} \quad \frac{R}{2\omega L} \text{ Hz}$$

(c) Low Pass filter

$$2R^2 = R^2 + (\omega L)^2$$
$$\omega = \frac{R}{L}$$