

Example

D9.1. Find the value of I_o in the network of Figure D9.1; assume an ideal op amp.

property of ideal amp.

$$V_- = V_+ = 12V$$

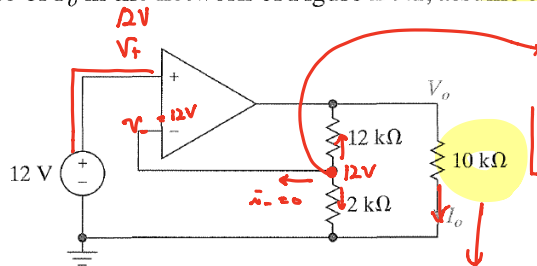


FIGURE D9.1

Ans: $I_o = 8.4 \text{ mA}$.

$$V_+ = V_-$$

$$I_+ = I_- = 0$$

$$\frac{12 - V_o}{12k} + \frac{12}{2k} + 0 = 0$$

$$12 - V_o + 6 \cdot 12 = 0$$

$$V_o = 84V$$

$$I_o = \frac{84}{10k} = 8.4 \text{ mA}$$

Example

D9.2 Figure D9.2 is a differential voltage amplifier, often called an instrumentation amplifier, which has a high input resistance, and therefore more appropriate for applications with a high source resistance (like the medical applications previously mentioned). It is also commonly used to measure sensor outputs from bridge circuits. Assuming ideal op amps; what is an expression for the output voltage in terms of the two inputs?

At node A

KCL

$$\textcircled{1} \frac{v_1 - v_o'}{R_1} + \frac{v_1 - v_2}{R_G} + \frac{v_1 - v_2}{R_2} + 0 = 0$$

At node B

$$\textcircled{2} \frac{v_2 - v_o'}{R_1} + \frac{v_2 - v_1}{R_G} + \frac{v_2 - v_o'}{R_2} = 0$$

①-② = 하면

$$\frac{v_1}{R_1} + \frac{1}{R_G} (v_1 - v_2) + \frac{v_1}{R_2} - \frac{v_2}{R_2} - \frac{1}{R_G} (v_2 - v_1) - \frac{v_2}{R_1} = \frac{v_o}{R_2}$$

$$\frac{1}{R_1} (v_1 - v_2) + \frac{2}{R_G} \cdot (v_1 - v_2) + \frac{1}{R_2} (v_1 - v_2) = \frac{v_o}{R_2}$$

Ans:

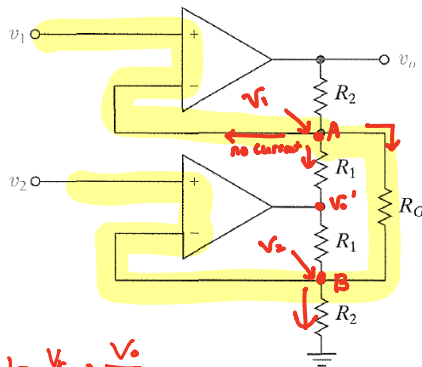



FIGURE D9.2

$$v_o = (v_1 - v_2) \left[1 + \frac{R_2}{R_1} + \frac{2R_2}{R_G} \right]$$

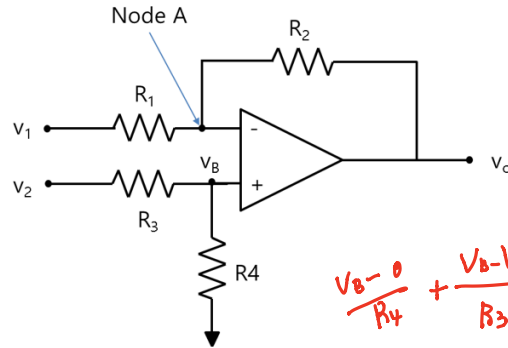Example

- Ex1

(10 points) Consider the following circuit including an ideal operational amplifier.



$$R_3 (V_B) + R_4 \cdot (V_B - V_2) = 0$$

$$V_B (R_3 + R_4) = R_4 \cdot V_2$$

$$\frac{V_B - 0}{R_4} + \frac{V_B - V_2}{R_3} + 0 = 0$$

$$V_B = \frac{R_4 \cdot V_2}{R_3 + R_4}$$

(a) (4 points) Find v_B in terms of v_2 , R_3 , and R_4 .

(b) (6 points) Apply KCL on node A and Find v_o in terms of v_1 , v_2 , R_1 , R_2 , R_3 , and R_4 .

$$\frac{V_A - V_o}{R_2} + \frac{V_A - V_1}{R_1} = 0$$

$$V_A = V_B$$

$$R_1 (V_A - V_o) + R_2 (V_A - V_1) = 0$$


$$V_o = \frac{V_A + R_2 V_A - R_2 V_1}{\frac{R_1}{R_1}}$$

$$V_o = \frac{R_4 - R_2}{R_3 + R_4} + \frac{R_2 \cdot \frac{R_4 \cdot V_2}{R_3 + R_4}}{R_1} - \frac{R_2 \cdot V_1}{R_1}$$

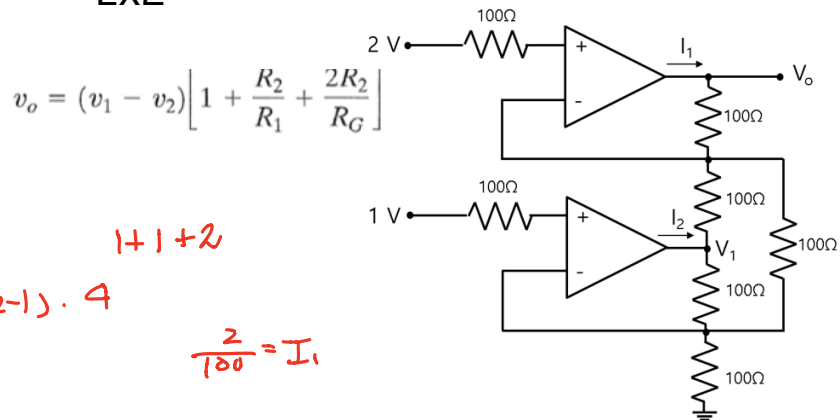Example

• Ex2

(10 points) Consider the following circuit including an ideal operational amplifier.



$$v_o = (v_1 - v_2) \left[1 + \frac{R_2}{R_1} + \frac{2R_2}{R_G} \right]$$

$$1+1+2$$

$$(2-1) \cdot 4$$

$$\frac{2}{100} = I_1$$

$$\frac{(1-2)}{100}$$

(a) (4 points) Find V_o and V_1 .

$$V_o = 4V \quad V_1 = 1V$$

(b) (3 points) Find I_1 .

$$0.02A$$

(c) (3 points) Find I_2 .

$$-0.01A$$

Example

9.14. For the circuit shown in Figure P9.14, assume the voltage source is given by $v_s = 0.1 \cos(2000t)$ V.

- Write an expression for v_o , the output voltage across the load resistor, R_L ?
- What is the maximum current through R_L ?
- What is the maximum current from the output of the op amp?

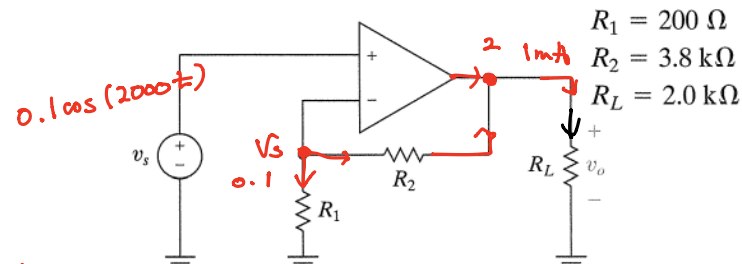


FIGURE P9.14

KCL

$$\frac{v_s}{R_1} + \frac{v_s - v_o}{R_2} = 0$$

(a). $\therefore v_o = (1 + \frac{R_2}{R_1}) \cdot v_s = (1 + \frac{3.8k}{200}) \cdot v_s$
 $= 20 v_s = 2 \cos(2000t)$

9.24. Determine the output voltage, v_o , across R_L in Figure P9.24, assuming an ideal op amp.

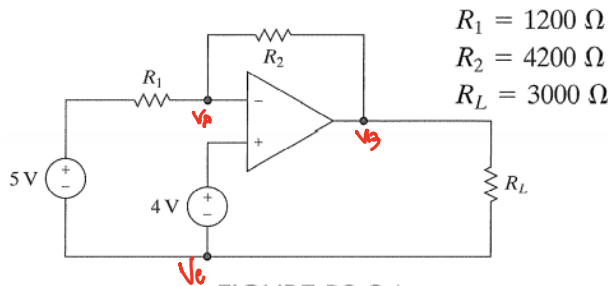


FIGURE P9.24

9. 14

- (a) Write an expression for v_o , the output voltage across the load resistor, R_L ?

KCL 적용하면.

$$\frac{V_s - 0}{R_1} + \frac{V_s - V_o}{R_2} = 0$$

$$V_o = \left(1 + \frac{R_2}{R_1}\right) \cdot V_s = \left(1 + \frac{3.8k}{200}\right) V_s$$

$$= 20 V_s = 2 \cos(2000t)$$

- (b) What is the maximum current through R_L ?

$$\frac{2 \cos(2000t)}{2k} \quad I_{max} = \frac{2}{2k} = 1mA$$

- (c) What is the maximum current from the output of the op amp?

$$V_s = \frac{1}{10} \cos(2000t) = \max = 0.1$$

$$V_o = \max = 2$$

$$I_{max} = \frac{2 - 0.1}{3.8k} = \frac{1.9}{3.8k} = 0.5mA + 1mA = 1.5mA$$

$$\frac{V_o - V_s}{R_2}$$

9. 24

$$\frac{V_A - 5}{R_1} + \frac{V_B - V_A}{R_2} + 4 = 0$$

$$\frac{V_A - 5}{1200} + \frac{V_B - V_A}{4200} + 4 = 0$$

$$\frac{V_B + 4}{R_L} + \frac{V_B - V_A}{R_2} = 0$$

Example

$$v_o = -\left[\frac{R_2}{R_{1A}}v_{iA} + \frac{R_2}{R_{1B}}v_{iB}\right]$$

- 9.31.** For the circuit in Figure P9.31, determine an expression for the output voltage, v_o , in terms of the input voltages, v_A , v_B , and v_C ; assume an ideal op amp.

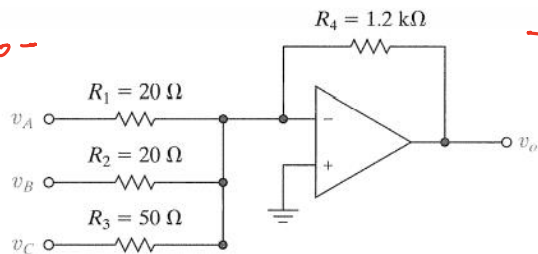


FIGURE P9.31

$$v_o = -60v_A - 60v_B - 24v_C$$

- 9.41.** Determine the maximum gain and bandwidth of the filter shown in Figure P9.41; assume an ideal op amp.

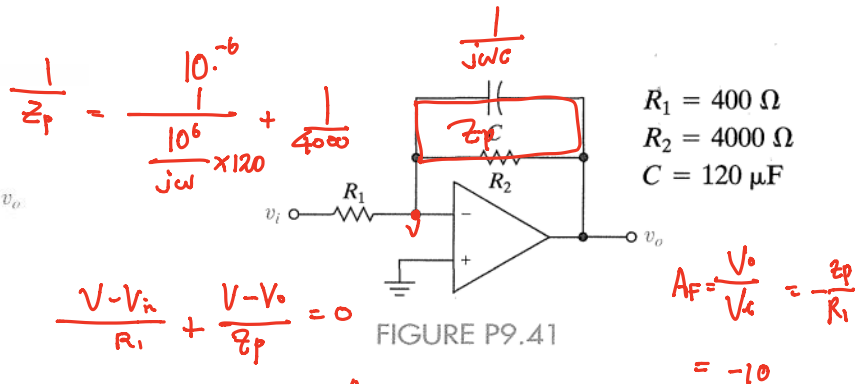


FIGURE P9.41

$$\text{Max gain} = -10$$

$$\text{BW} = 2.08 \text{ rad/s}$$

$$= 0.33 \text{ Hz}$$