
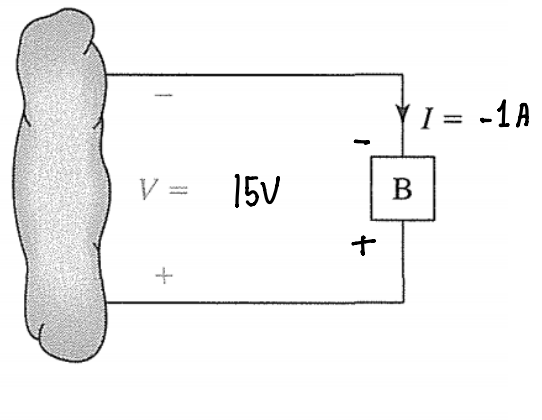




$$A (\text{암페어}) = I (\text{current})$$

1. Assign values to  $V$  and  $I$  in element B so that it is equivalent to element A (see Figure 1).



$$V = I \cdot R$$

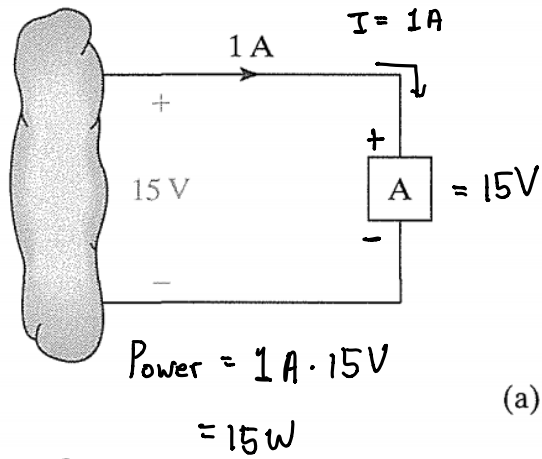

(a)

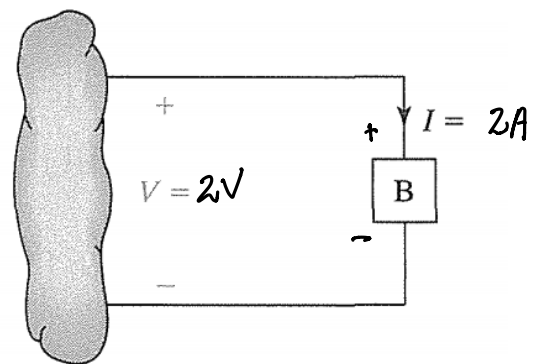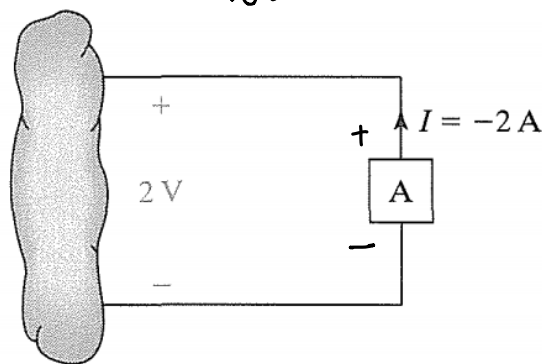


(b)

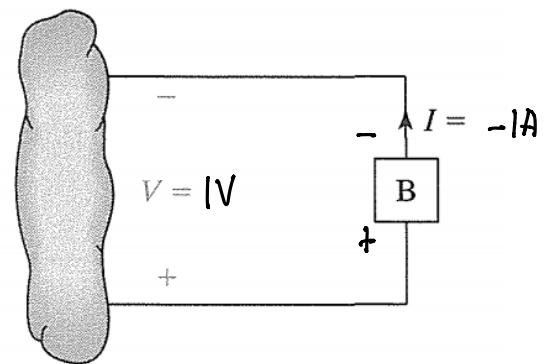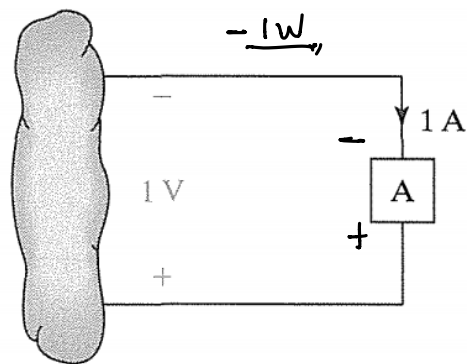


(c)

Figure 1

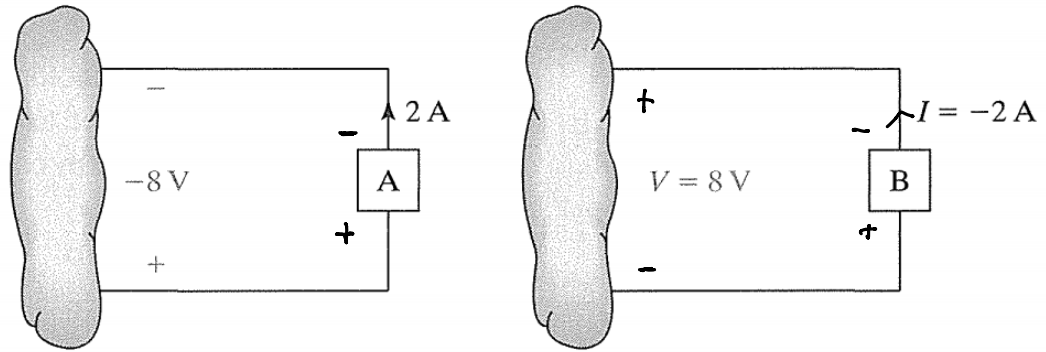
2. Assign directions to currents and polarities to voltages in element B so it is equivalent to element A (see Figure 2)



(a)

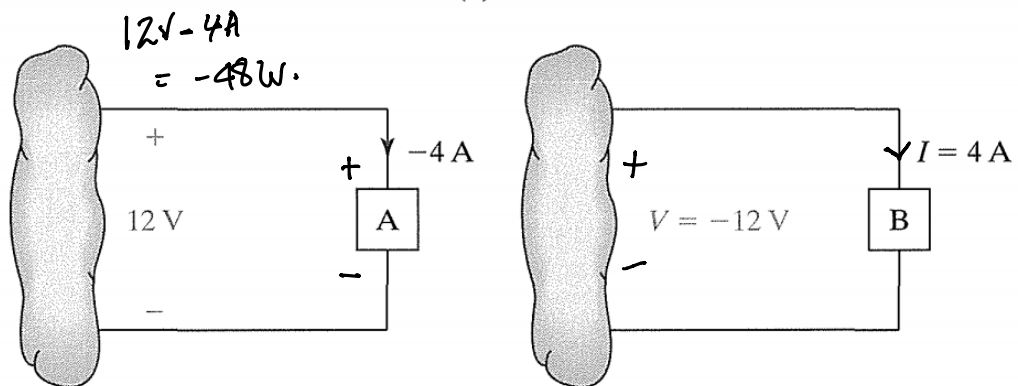

(b)

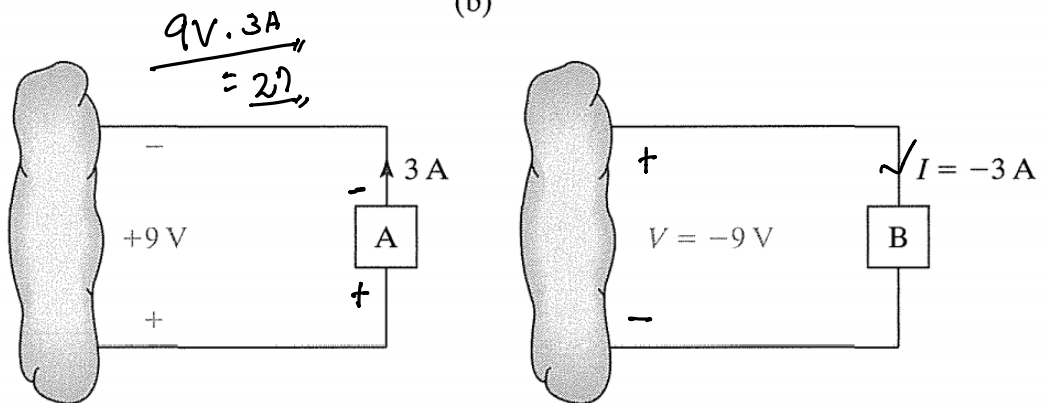

(c)

Figure 2

3. In the elements of Figure 3, determine for each if they are supplying power or absorbing power and the magnitude of the power being transferred.

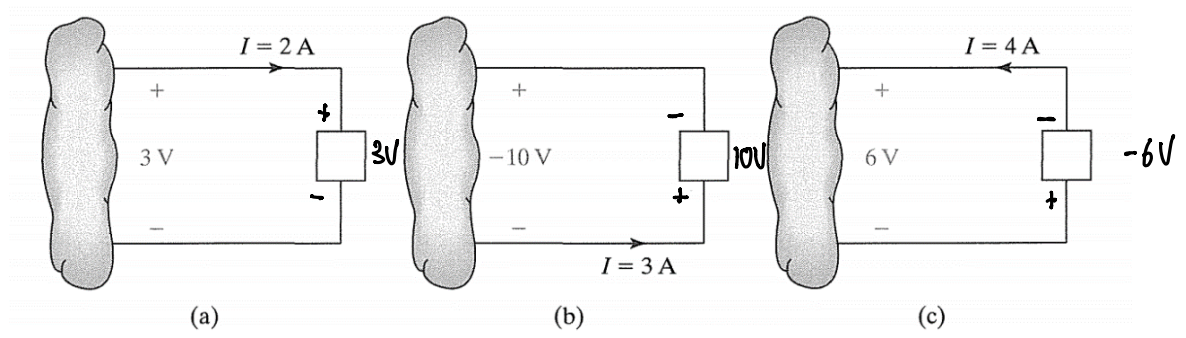


Figure 3

(a)  $\text{Power} = I \cdot V$   
 $= 2\text{A} \cdot 3\text{V}$   
 $= 6\text{W}$

$6\text{W} > 0 \Rightarrow \underline{\text{Absorbing Power}}$

(b)  $P = 10\text{V} \cdot 3\text{A} = 30\text{W}$   
 $30\text{W} > 0 \Rightarrow \underline{\text{Absorbing Power}}$

(c)  $P = -6\text{V} \cdot 4\text{A} = -24\text{W}$   
 $-24\text{W} < 0 \Rightarrow \underline{\text{Supplying Power}}$

4. In Figure 4 determine for each element whether it is supplying or absorbing power. If all the energy absorbed is dissipated as heat dissipated (in joules) over a period of one hour for each of the circuits shown.

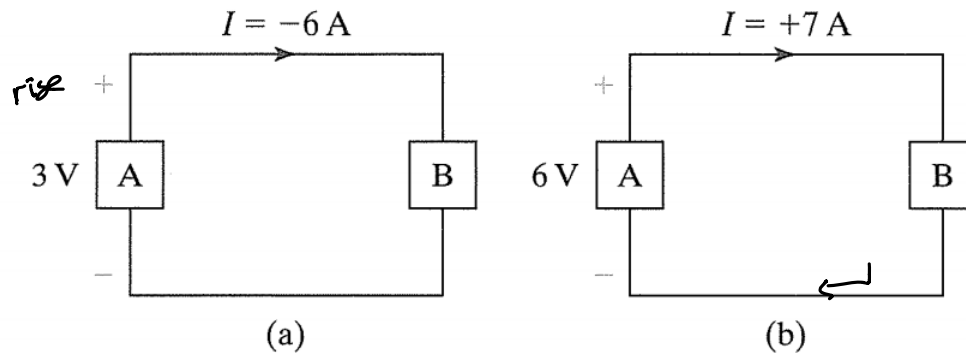


Figure 4

$$(a) \quad P_A = 3V \cdot 6A = 18W > 0 \Rightarrow \text{Absorbing power}$$

$$P_B = 3V \cdot -6A = -18W < 0 \Rightarrow \text{Supplying power.}$$

$$(b) \quad P_A = 6V \cdot -7A = -42W < 0 \Rightarrow \text{Supplying power.}$$

$$P_B = 6V \cdot 7A = 42W > 0 \Rightarrow \text{Absorbing power}$$

5. A heater element draws 2.0 A when connected to a 120 V source. Calculate both the resistance of the element and the power absorbed in the form of heat.

$$R = \frac{V}{I} = \frac{120}{2.0} = 60 \Omega$$

$$P = I \cdot V = 2.0 \times 120 = 240 \text{ W}$$

6. A speaker is a device that converts electrical energy into sound energy. Assume the internal resistance of a speaker is typically  $8\Omega$ . The speaker's power rating is maximum power that can be delivered to it without damage. Therefore, determine the maximum safe current that can be delivered to a stereo speaker with internal resistance of  $8\Omega$  and a power rating of 200 watts.

$$\underline{8\Omega = \frac{V}{A}}$$

$$\underline{200 = I \cdot V}$$

$$\boxed{I = 5A}$$

$$P = I \cdot V$$

$$200 = VA$$

$$8\Omega \cdot A = V$$

$$8V \frac{V}{8} = \frac{200}{V}$$

$$\underline{V = 40}$$

$$\underline{V^2 = 1600}$$

7. Find  $I$  and  $V_o$  in the network in Figure 5.

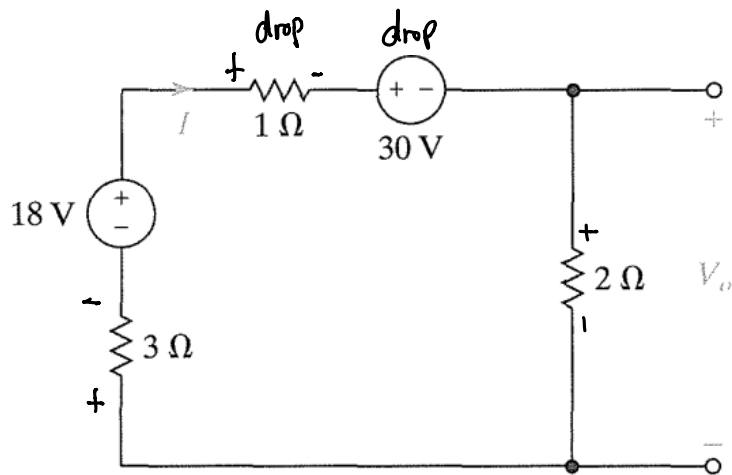


Figure 5

$$R_s = 6\Omega$$

$$18 - 30 = I \cdot 1 + 2I + 3I$$

$$6I = -12$$

$$I = -2A$$

$$V_o = -2A \cdot 2 = -4V$$

8. Find  $V$ ,  $I_1$ ,  $I_2$ , and  $P_{6\Omega}$  in the network in Figure 6.

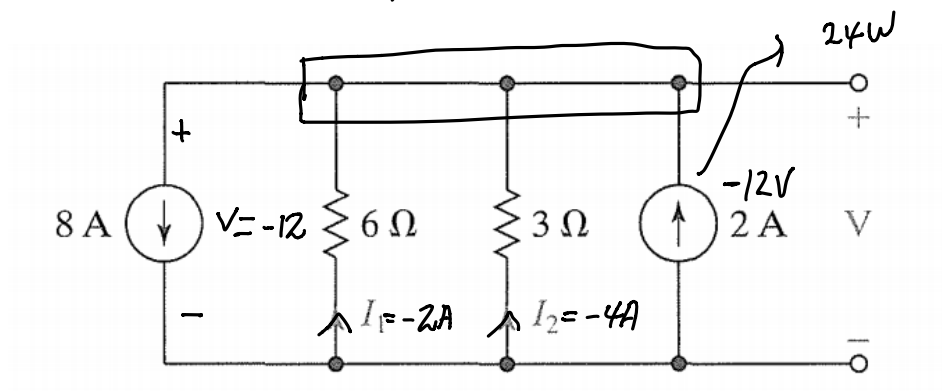


Figure 6

$$I = \frac{V}{R}$$

$$-8 + 2 + (I_1 + I_2) = 0$$

$$I_1 + I_2 = 6$$

$$-V(t) \left( -\frac{1}{6} - \frac{1}{3} \right) = 6$$

$$-\frac{V(t)}{2} = +6 \quad \underline{V(t) = -12}$$

$$\underline{I_1 = 2A}$$

$$\underline{I_2 = 4A}$$

$$P_{6\Omega} = I \cdot V$$

$$= -2A \cdot -12 = \underline{24W}$$



9. Find the equivalent resistance at the terminals  $A - B$  in the network in Figure 7.


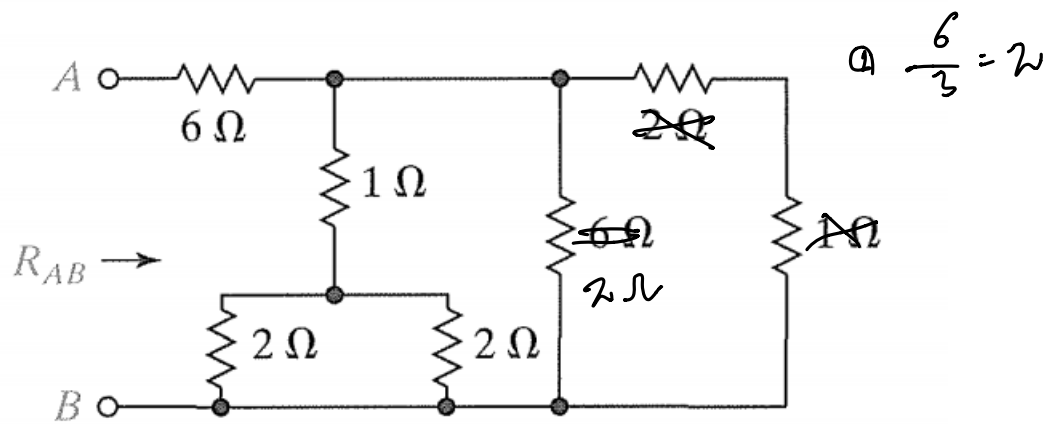
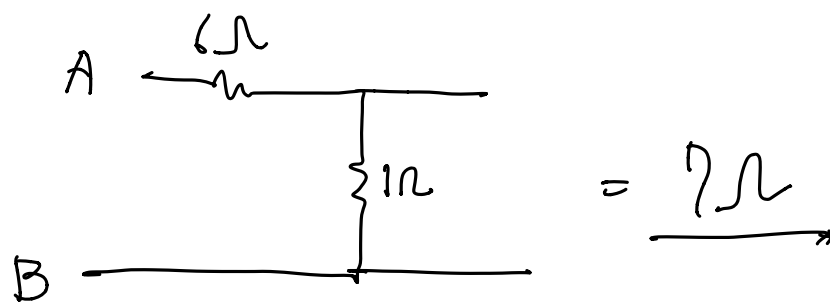
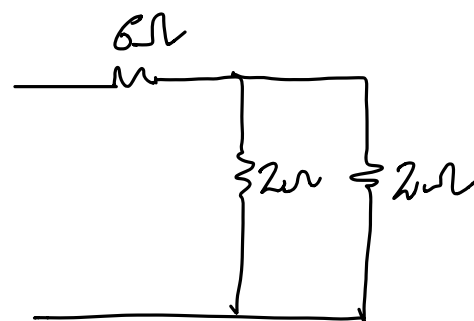


Figure 7

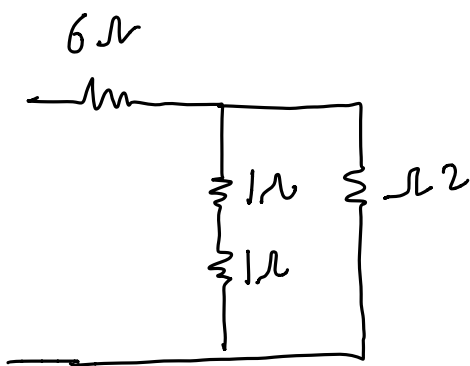

10. Find the resistance at terminals  $A - B$  in the network in Figure 8


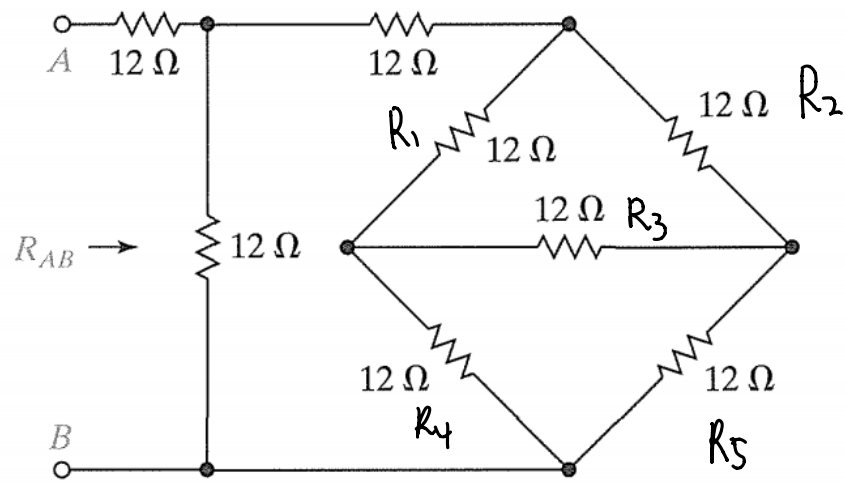


Figure 8

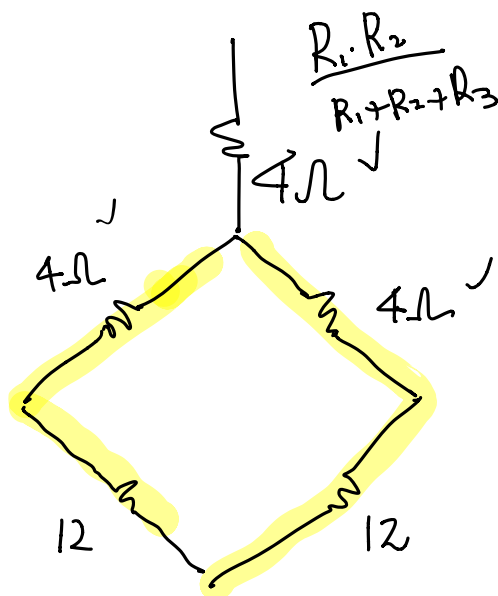

$$\frac{R_1 \cdot R_2}{R_1 + R_2 + R_3} = \frac{144}{36} = 4\Omega$$

$$\frac{1}{R_T} = \frac{1}{16} + \frac{1}{16} = \frac{1}{8}$$

