

Example

D5.1. Find the average power absorbed by each resistor in the network in Figure D5.1.

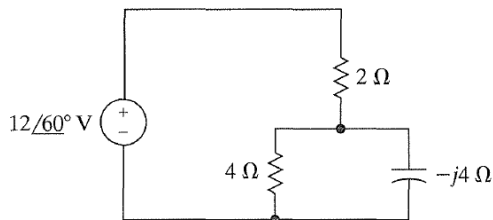


FIGURE D5.1

$$\frac{1}{Z_p} = \frac{1}{4} + \frac{1}{-j4} \quad \frac{1}{4} + \frac{j}{4}$$

$$Z_p = \frac{4}{1+j} = 2-j$$

$$4-j = 4.47 \angle -26.5^\circ$$

$$I = \frac{12}{Z} = 2.68 \angle 86.5^\circ$$

$$I_{4\Omega} = I \times \frac{-j4}{4-j4} = I \times \frac{1-j}{2}$$

$$= 2.68 \times \frac{\sqrt{2}}{2} = 1.9$$

$$P_{4\Omega} = \frac{1}{2} \times (4.9)^2 \times 4 = 7.14 \text{ W}$$

$$P_{2\Omega} = \frac{1}{2} \times (2.68)^2 \times 2 = 7.18 \text{ W}$$

Ans: $P_{2\Omega} = 7.18 \text{ W}$, $P_{4\Omega} = 7.14 \text{ W}$.

$$I_{2\Omega} = 2.68 \times 1 = 2.67$$

Example

D5.2. Given the network in Figure D5.2, find the average power absorbed by each passive circuit element and the total average power supplied by the current source.

$$I_{3\Omega} + I_{4\Omega} = 10 \angle 30^\circ$$

$$I_{4\Omega} = \frac{4+j2}{7+j2} = 6.14 \angle 0.21$$

$$I_{3\Omega} = \frac{3}{7+j2} = 4.12 \angle 0.245$$

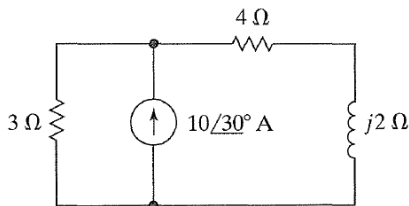


FIGURE D5.2

Ans: $P_{3\Omega} = 56.62 \text{ W}$, $P_{4\Omega} = 33.95 \text{ W}$, $P_L = 0$, $P_{cs} = -90.50 \text{ W}$.

$$P_{3\Omega} = \frac{1}{2} \times (4.14)^2 \times 3 = 56.62 \text{ W}$$

$$P_L = 0$$

$$P_{4\Omega} = \frac{1}{2} \times (4.12)^2 \times 4 = 33.95 \text{ W}$$

$$P_{cs} = -(56.62 + 33.95) = -90.57 \text{ W}$$

Example

D5.3. Compute the rms value of the voltage waveform shown in Figure D5.3.

$$v(t) - 0 = 2 \times t \quad \frac{4}{2}$$

$$v(t) = 2t$$

$$v(t) = \begin{cases} 2t & 0 \leq t < 2 \\ 0 & 2 \leq t < 4 \end{cases}$$

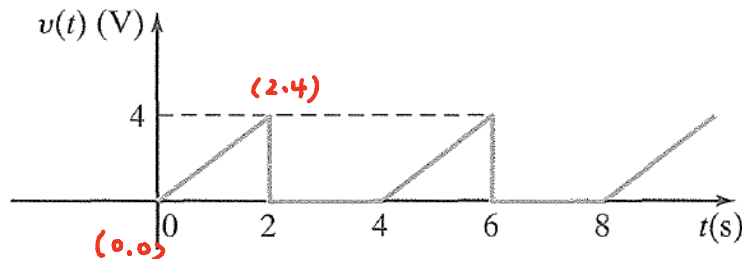


FIGURE D5.3

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$= \sqrt{\frac{1}{4} \left(\int_0^2 (2t)^2 dt + \int_2^4 0^2 dt \right)}$$


Ans: $V_{\text{rms}} = 1.633 \text{ V rms.}$

$$= \left[\frac{t^3}{3} \right]_0^2 = \sqrt{\frac{8}{3}} = \underline{\underline{1.633}}$$

Example

D5.5. An industrial load consumes 100 kW at 0.707 PF lagging. The 60 Hz line voltage at the load is $480 \angle 0^\circ$ V rms. The transmission line resistance between the power company's transformer and the load is 0.1Ω . Determine the power savings that could be obtained if the PF is changed to 0.94 lagging.

Ans: Power saved is 3.771 kW.

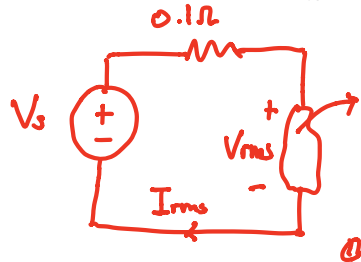

$$P = 100 \text{ kW} = 10^5 \text{ W}$$

$$480 \cdot I_{rms} \times 0.707 = 10^5$$

$$I_{rms} = 294.67$$

$$P_{0.1\Omega} = I_{rms}^2 \times 0.1 = (294.67)^2 \times 0.1 = 8.68 \times 10^3 \text{ W}$$

$$480 \times I_{rms} \times 0.94 = 10^5$$

$$\textcircled{2} \quad I_{rms} = 221.63$$

$$P_{0.1\Omega} = 221.63^2 \times 0.1 = 4.91 \times 10^3 \text{ W}$$

$$(8.68 - 4.91) = \underline{3.77 \text{ kW}}$$

Example

D5.6. An industrial load operates at 20 kW, 0.8 PF lagging with a line voltage of $220\angle 0^\circ$ V rms. Construct the power triangle for the load.

Ans:

$$P = V_{rms} \cdot I_{rms} \cdot \cos(\theta_v - \theta_i)$$

$$\theta_v - \theta_i = \cos^{-1} 0.8$$
$$\approx 36.67^\circ$$

$$S = 20 \text{ kW} \times \frac{1}{\cos 36.67^\circ} = 25 \text{ kVA}$$

$$Q = 20 \text{ kW} \times \tan 36.67^\circ = 15 \text{ kvar}$$

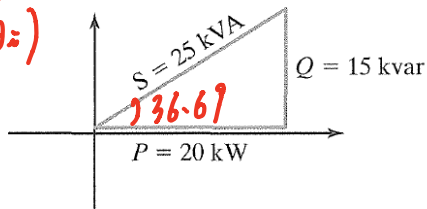


FIGURE D5.6