

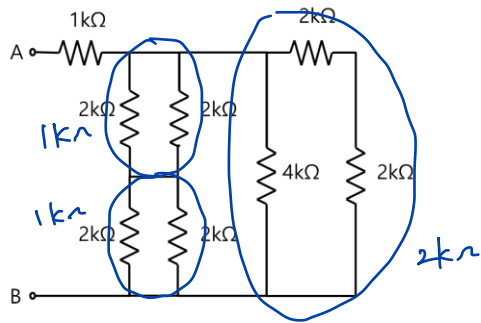


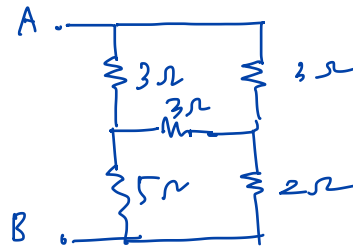1. Find the resistance between terminals A-B in the following circuit.




$$\therefore R_{AB} = 2\text{k}\Omega$$

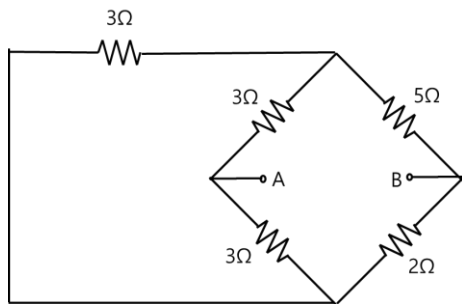2. Find the resistance between terminals A-B in the following circuit.




$$\frac{3 \cdot 3}{3 + 3 + 3} = 1$$

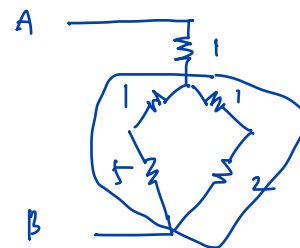

$$\frac{1}{R_p} = \frac{1}{6} + \frac{1}{3} = \frac{1+2}{6}$$

$$\therefore R_{AB} = 3\Omega$$

3. Consider the following circuit.

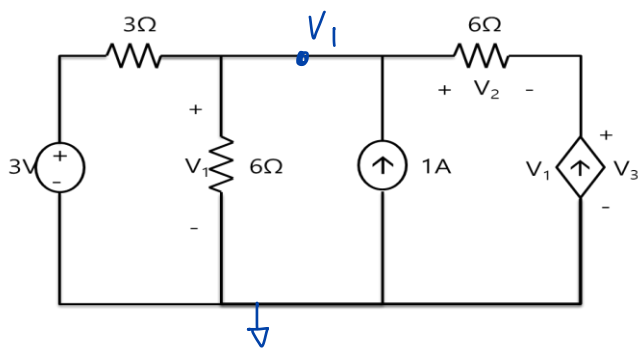

(a) Find V_1 and V_2 .

$$\frac{V_1 - 3}{3} + \frac{V_1}{6} - 1 - V_1 = 0.$$

$$2V_1 - 6 + V_1 - 6 - 6V_1 = 0.$$

$$-3V_1 = 12 \quad \therefore V_1 = \underline{-4V}.$$

$$V_2 = -V_1 \cdot 6 = \underline{24V}.$$


(b) Find V_3 and the power absorbed or supplied by the dependent current source. (If $P < 0$, the power is supplied. If $P > 0$, the power is absorbed)

$$V_1 = V_2 + V_3$$


$$-4 = 24 + V_3 \quad \therefore V_3 = \underline{-28V}.$$

$$P_{\diamond} = -V_1 \cdot V_3 = -(-4) \cdot (-28) = -112W. \quad (\text{supplied})$$

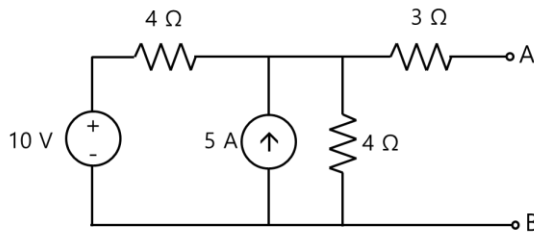4. (a) Find Thevenin equivalent circuit between terminals A-B of the following circuit.




① For V_{oc}

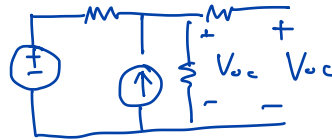

$$\frac{V_{oc} - 10}{4} - 5 + \frac{V_{oc}}{4} = 0.$$

$$2V_{oc} - 10 = 20 \quad \therefore V_{oc} = 15V.$$

② For I_{sc}

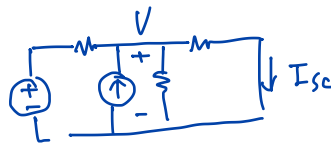


$$\frac{V - 10}{4} - 5 + \frac{V}{4} + \frac{V}{3} = 0.$$

$$3V - 30 - 60 + 3V + 4V = 0 \quad V = 9V$$


$$\therefore I_{sc} = 3A.$$
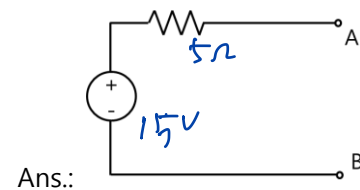
$$\therefore R_{Th} = \frac{15}{3} = 5\Omega$$




Ans.:

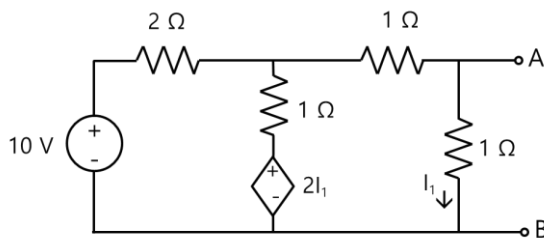(a) Find Norton equivalent circuit between terminals A-B of the following circuit.



① For V_{oc}

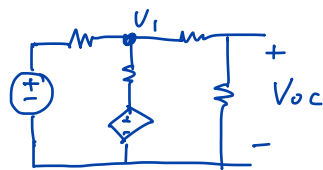


$$\frac{V_1 - 10}{2} - \frac{V_1 - 2I_1}{1} + \frac{V_1}{2} = 0.$$

$$I_1 = \frac{V_1}{2}.$$

$$V_1 = 5V. \quad V_{oc} = \frac{5}{2}V.$$

② For I_{sc}

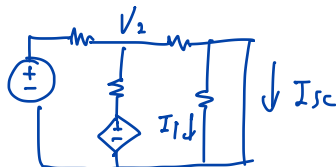


$$\frac{V_2 - 10}{2} + \frac{V_2}{1} + \frac{V_2}{1} = 0.$$

$$V_2 - 10 + 4V_2 = 0 \quad \therefore V_2 = 2V.$$

$$I_{sc} = 2A.$$

$$R_{Th} = \frac{5/2}{2} = 5/4$$

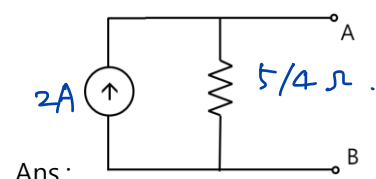

Ans.: