

# Final Exam

Jun. 18, 2019

Time: 10:30 ~ 11:50



Name \_\_\_\_\_

ID Number \_\_\_\_\_

Signature \_\_\_\_\_


- If there is no answer, you can get only partial credit for your work.
- Don't forget the units of your answers

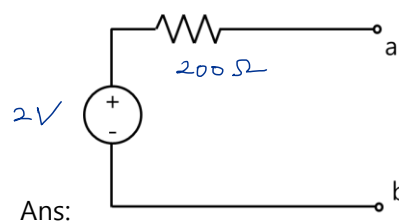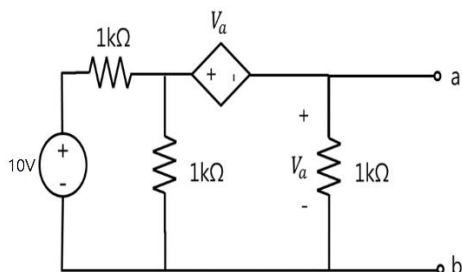1. (10 points) Find the Thevenin equivalent circuit between terminal a-b of the following circuit.




Ans:

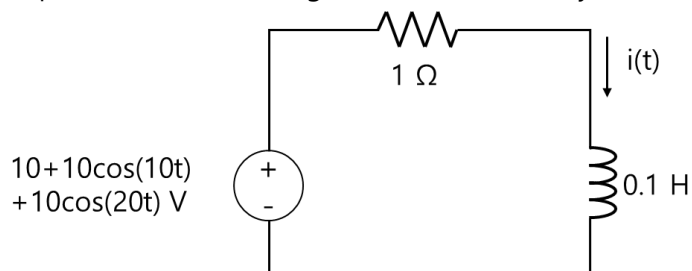2. (10 points) In the following ~~LC~~ circuit, find steady-state  $i(t)$ . ( $\frac{1}{1+j} \approx 0.7\angle-45^\circ$ ,  $\frac{1}{1+2j} \approx 0.45\angle-63^\circ$ )




Ans.:  $10 + 7 \cos(10t - 45^\circ) + 4.5 \cos(20t - 63^\circ)$

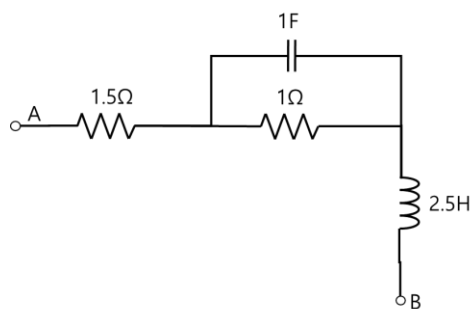3. (a) (5 points) Find the total impedance between terminals A and B in the following figure.



Ans.:  $1.5 + \frac{1}{1+j\omega} + j2.5\omega$

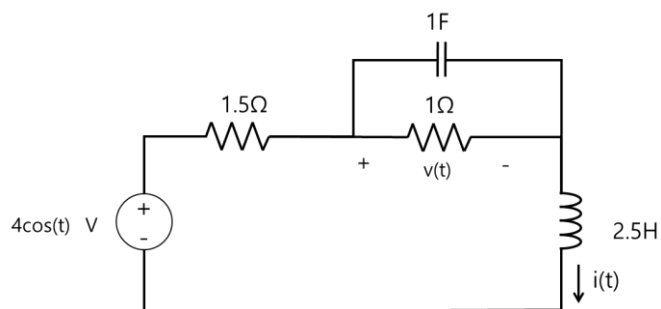For (b) and (c), consider the following RLC circuit.




- (b) (5 points) Find steady-state  $i(t)$ . ( $\frac{1}{1+j} \approx 0.7\angle-45^\circ$ )

Ans.:  $1.4 \cos(t - 45^\circ)$

- (c) (5 points) Find steady-state  $v(t)$ .

Ans.:  $\cos(t - 90^\circ)$

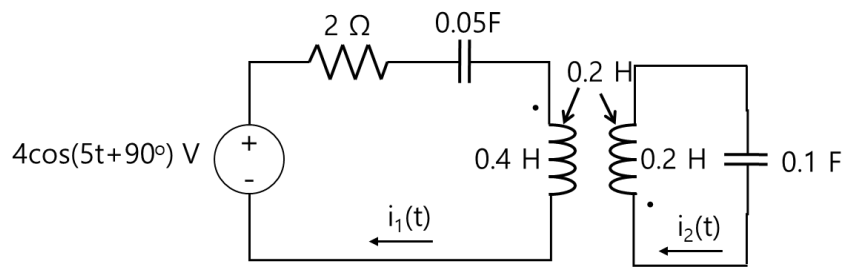4. (10 points) Consider the following circuit.




Complete the following equations about phasor currents,  $\mathbf{I}_1$  and  $\mathbf{I}_2$  of  $i_1(t)$  and  $i_2(t)$ , respectively.

$$\boxed{2-j} \mathbf{I}_1 + \boxed{j} \mathbf{I}_2 = \boxed{4j}$$

$$\boxed{j} \mathbf{I}_1 + \boxed{-j} \mathbf{I}_2 = 0$$

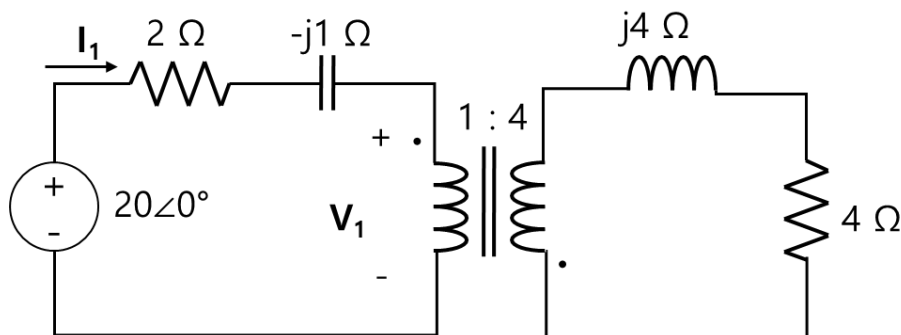5. (10 points) Consider the following circuits with an ideal transformer.




Complete the following equations about phasor currents,  $\mathbf{I}_1$  and  $\mathbf{V}_1$ .

$$\boxed{2-j} \mathbf{I}_1 + \boxed{1} \mathbf{V}_1 = \boxed{20}$$

$$\boxed{-C(1+j)} \mathbf{I}_1 + \boxed{4} \mathbf{V}_1 = 0$$

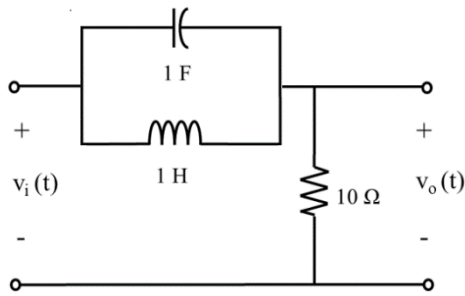6. (15 points) In the following circuit, the input signal is  $v_i(t)$  and the output signal is  $v_o(t)$ .



- (a) (6 points) Find the frequency response of  $\mathbf{V}_o(j\omega)/\mathbf{V}_i(j\omega)$ .

$$\frac{10}{10 + \frac{j\omega}{1-\omega^2}} = \frac{10(1-\omega^2)}{10(1-\omega^2) + j\omega}$$

Ans.: \_\_\_\_\_

- (b) (3 points) Find the magnitude of the frequency response.

$$\text{Ans.: } \frac{|10(1-\omega^2)|}{\sqrt{100(1-\omega^2)^2 + \omega^2}}$$


- (c) (3 points) Find the phase of the frequency response.

$$\text{Ans.: } \left. \begin{array}{l} \pi - \tan^{-1} \frac{\omega}{10(1-\omega^2)} \\ - \tan^{-1} \frac{\omega}{10(1-\omega^2)} \end{array} \right\} \begin{array}{l} \omega^2 > 1 \\ \omega^2 < 1 \end{array}$$

- (d) (3 points) Determine the type of the filter. (low-pass filter, high-pass filter, bandpass filter, or band-rejection filter)

Ans.: band-rejection filter

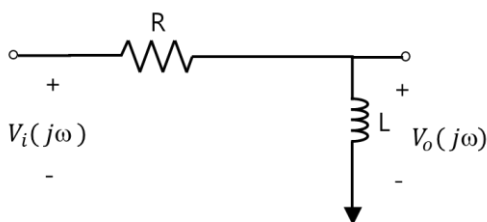7. (10 points) Consider the following circuit.



- (a) (4 points) Find the frequency response,  $\mathbf{V}_o(j\omega)/\mathbf{V}_i(j\omega)$ .

$$\text{Ans.: } \frac{j\omega L}{R + j\omega L} = \frac{1}{1 + \frac{R}{j\omega L}}$$


- (b) (3 points) Find 3 dB ~~bandwidth~~ frequency in the unit of rad/s.

$$\text{Ans.: } \frac{R}{L}$$

- (c) (3 points) Find 3 dB ~~bandwidth~~ frequency in the unit of Hz.


$$\text{Ans.: } \frac{R}{2\pi L}$$

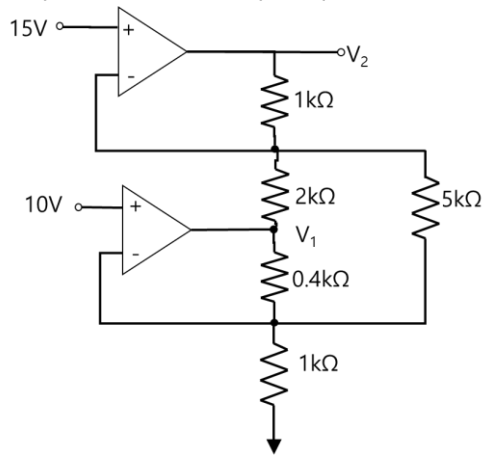8. (10 points) The two op amps in the following circuit are ideal. Calculate  $v_1$  and  $v_2$ .



Answers:  $v_1 = 13.6V$ ,  $v_2 = 4.7V$ .

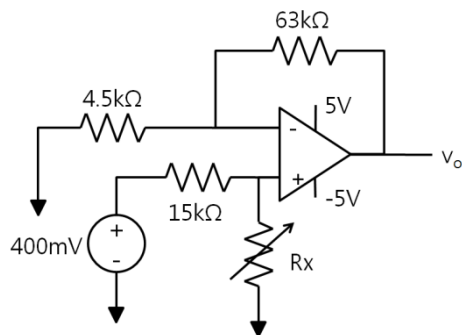9. (10 points) Consider the following circuit which contains an ideal op amp. The power supplies for the op amp are +5 V and -5V.



- (a) (5 points) Find  $v_0$  when  $R_x$  is 15 kΩ.

Answers:  $v_0 = 3V$ .

- (b) (5 points) How large can  $R_x$  be before the amplifier saturates?

Answers:  $R_x = 15k\Omega$ .