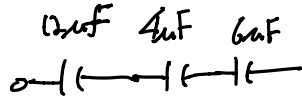


Example

D3.1. Find the total capacitance of the network in Figure D3.1.



$$\frac{1}{12} + \frac{1}{4} + \frac{1}{6} = \frac{1}{2}$$

$$\frac{4}{12} + \frac{2}{12}$$


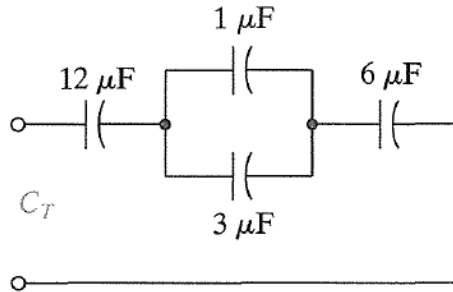


FIGURE D3.1

Handwritten result: $2\mu F$

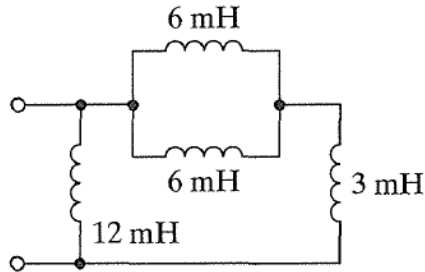
Example

D3.2. Find the total inductance in the network in Figure D3.2.



$$\underline{4 \text{ mH}}$$

FIGURE D3.2

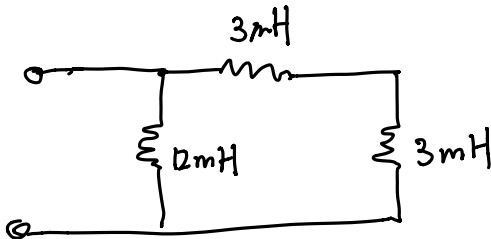

$$\frac{1}{12} + \frac{1}{6} = \frac{1}{4}$$

Example

D3.3. Find $i_o(t)$ and $v_o(t)$ for $t > 0$ in the network in Figure D3.3.



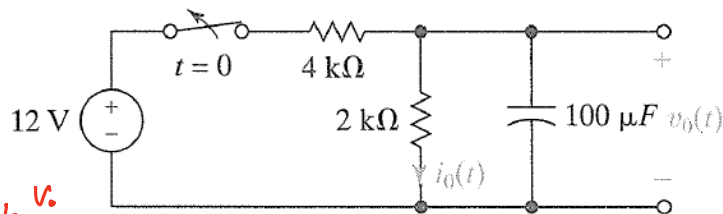


FIGURE D3.3

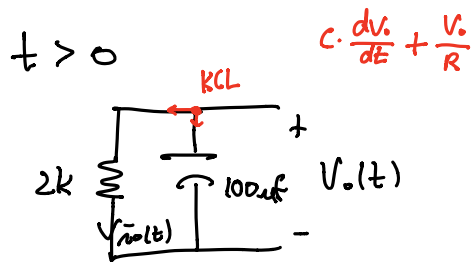

$$i_o(t) = \frac{v_o(t)}{2}$$

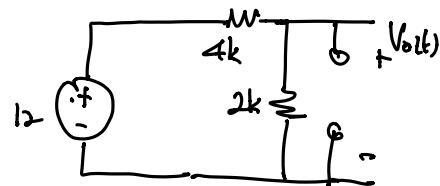

$$\frac{2}{4+2} \times 12 = 4V = K_2$$

$$\therefore t > 0 \quad v_o(t) = 4 \cdot e^{-t/0.2}$$

$$i_o(t) = 2e^{-t/0.2}$$

$$\textcircled{1} v_o(t) = K_1 + K_2 e^{-t/\tau}$$

$$\textcircled{2} \tau = R \cdot C = 0.2$$

$$\textcircled{3} v_o(t) = K_1 + K_2 e^{-t/0.2}$$

$$\textcircled{4} v_s = 0 = K_1$$

$$v_o(t) = K_2 e^{-t/0.2}$$


$$K_2 \quad v_o(t=0)$$

$$(-\frac{R}{L})t$$

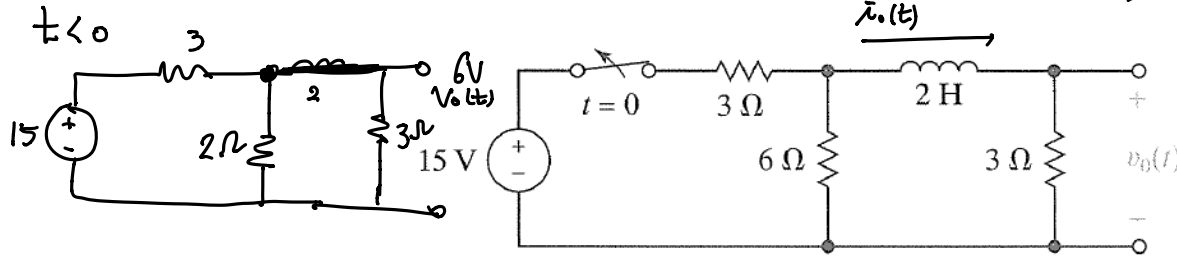Example

$$\frac{1}{6} + \frac{1}{3}$$

D3.4. Find $v_o(t)$ for $t > 0$ in the network in Figure D3.4.



$$\frac{2}{3+2} \times \frac{3}{1} = 6$$

$$V=6$$

$t > 0$

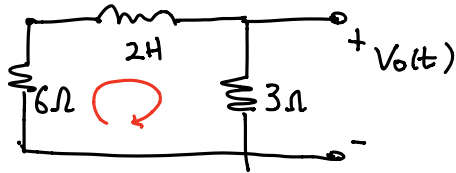


FIGURE D3.4

$$V = I \cdot R$$

$$\frac{1}{6} + \frac{1}{3} = \frac{1}{2}$$

$$\frac{6V}{3} = 2A$$

$$2e^{-4.5t} \times 3 = 6e^{-4.5t}$$

$$\tau = \frac{L}{R} = \frac{2}{9}$$

$$K_1 = 0$$

$$\bar{i}_o(t) = K_2 e^{-4.5t}$$

$$\bar{i}_o(t) = 2e^{-4.5t}$$

$$\bar{i}_o(t) = K_1 + K_2 e^{-t/\tau}$$

Example

D3.7. A series RLC circuit consists of $R = 2 \Omega$, $L = 1 \text{ H}$, and a capacitor. Determine the type of response exhibited by the network if (a) $C = 1/2 \text{ F}$, (b) $C = 1 \text{ F}$, and (c) $C = 2 \text{ F}$.

$$2\alpha = \frac{R}{L} = 2 = \underline{\alpha = 1}$$

$$x(t) = \tilde{x}(t)$$

$$\omega_0^2 = \frac{1}{LC} =$$

$$\begin{aligned} \text{(a)} \quad \alpha &= 1 & \alpha^2 &= 1 & \alpha^2 - \omega_0^2 &< 0 \\ \omega_0^2 &= 2 & \omega_0^2 &= 2 & \text{"underdamped"} \\ \omega_0 &= \pm\sqrt{2} \end{aligned}$$

$$\begin{aligned} \text{(b)} \quad \alpha^2 &= 1 & \text{"critically damped"} \\ \omega_0^2 &= 1 \end{aligned}$$

$$\begin{aligned} \text{(c)} \quad \alpha^2 &= 1 & \text{"overdamped"} \\ \omega_0^2 &= \frac{1}{2} \end{aligned}$$

Example

$$I = \frac{V}{R}$$

D3.9. The switch in the network in Figure D3.9 moves from position 1 to position 2 at $t = 0$. Find $v(t)$ for $t \geq 0$. $\frac{1}{RC} = 2$ $L = \frac{4}{3}$ $R = 1$

$$\alpha = 2$$

$$\omega_0 = \sqrt{3}$$

$$\frac{1}{4}(-k_1 e^{-t} - 3k_2 e^{-3t})$$

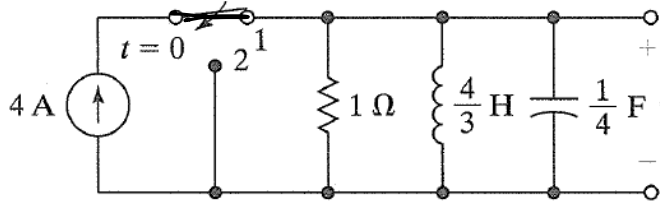


FIGURE D3.9

$$v(t) = -8e^{-t} + 8e^{-3t}$$

$$\frac{d^2 v(t)}{dt^2} + 4 \frac{dv(t)}{dt} + 3v(t) = 0$$

$$\rightarrow v(t) = k_1 e^{-t} + k_2 e^{-3t}$$

$$i(t) = \frac{3}{4}(-k_1 e^{-t} - \frac{1}{3}k_2 e^{-3t}) = -\frac{3}{4}k_1 e^{-t} - \frac{1}{4}k_2 e^{-3t}$$

$$\begin{aligned} v(0) &= 0 & k_1 &= -8 \\ i(0) &= 4 & k_2 &= 8 \end{aligned}$$